

# Capacitance

## I. Basic Concepts

- definition
- steady state behavior

## II. Capacitor Design


- capacitance vs. geometry
- materials & dielectrics

## **III. RC Circuits**

- dynamic behavior**
- charging/discharging**


	The student will be able to:	HW:
1	Define and calculate capacitance in terms of voltage and charge and solve related problems.	1 – 3
2	Solve steady-state problems involving series and parallel connections of capacitors and batteries.	4 – 6
3	Solve problems relating capacitance to geometry and dielectrics for parallel plate, cylindrical, and spherical capacitors.	7 – 17
4	Analyze RC circuits in terms of the appropriate differential equation and resulting exponential functions for charge, current, voltage, etc.	18 – 22

# Intermittent wiper controller.

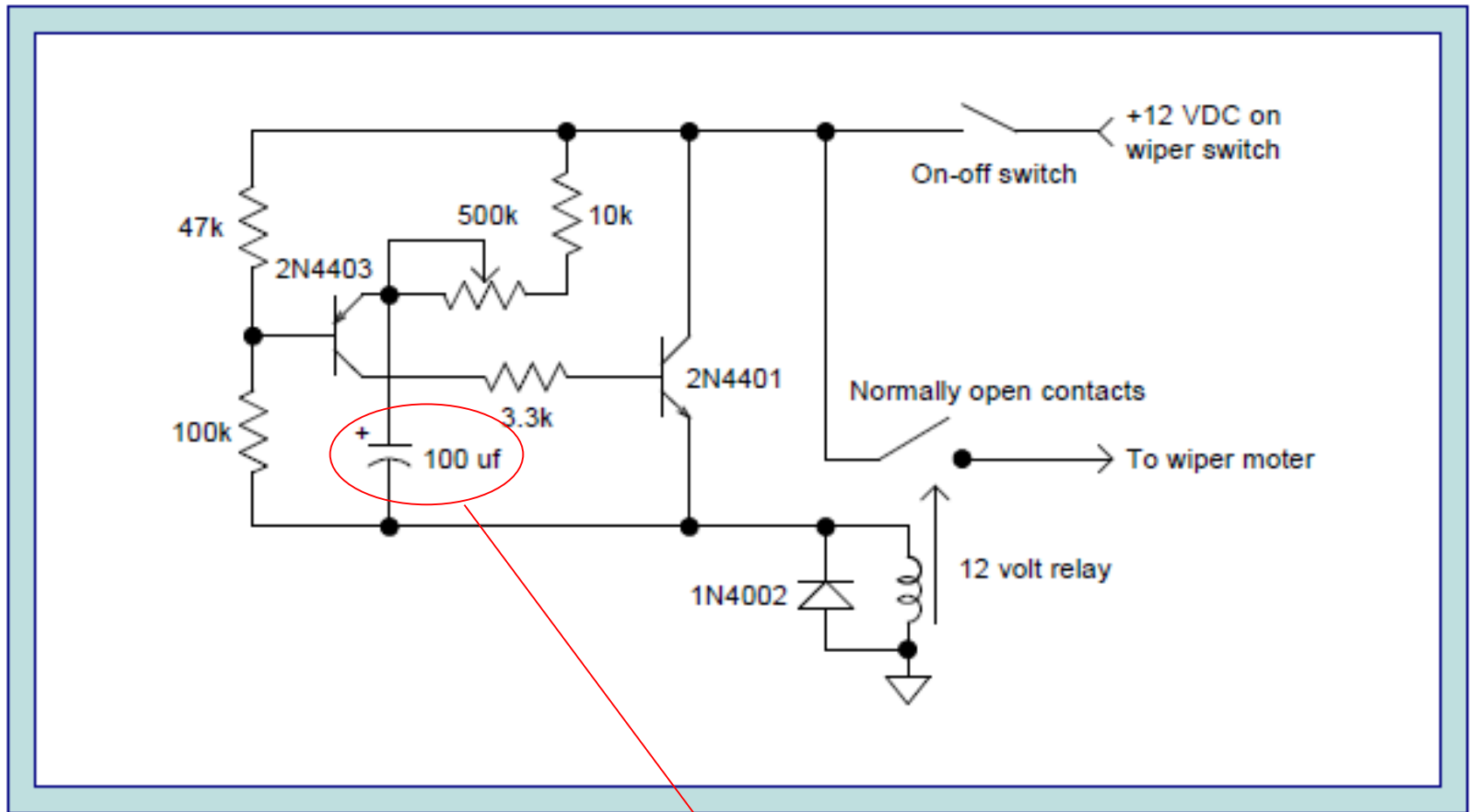


What is the role of the capacitor in this circuit?

# Intermittent wiper controller.

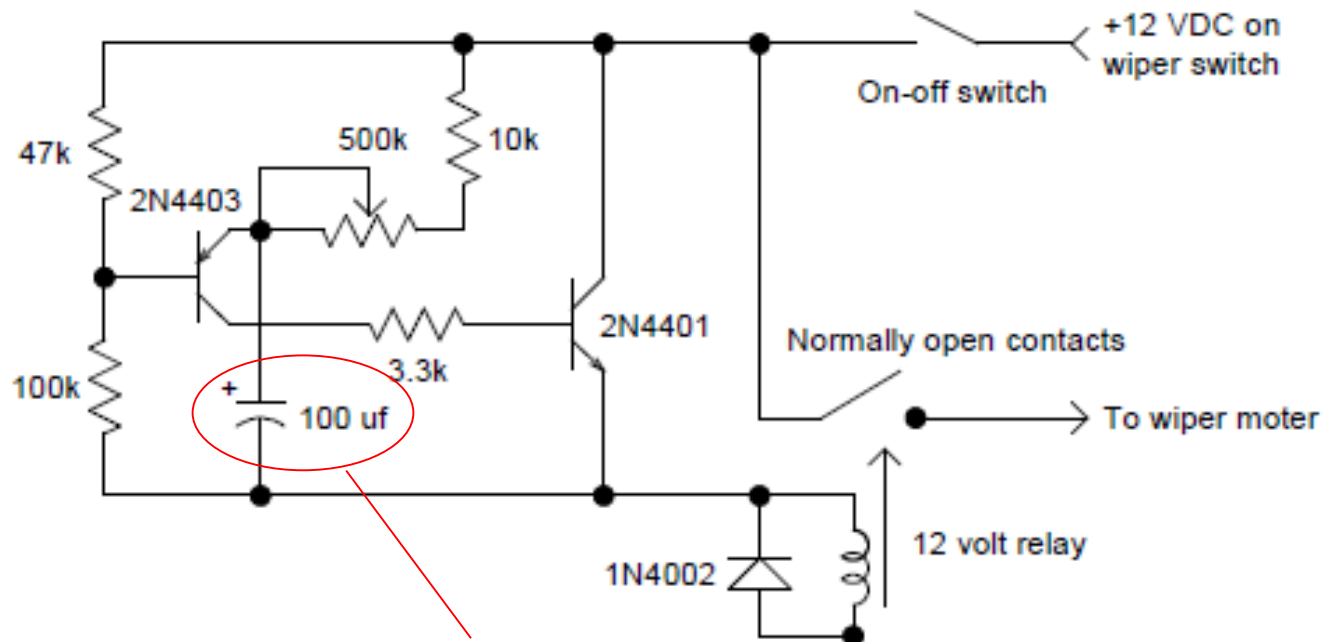

The wipers are turned on and off at a rate controlled and synchronized by the time it takes for the capacitor to charge and discharge. The time for this to happen can be adjusted with the variable 500 k $\Omega$  resistor. This is a good example of an application of an *RC* circuit.

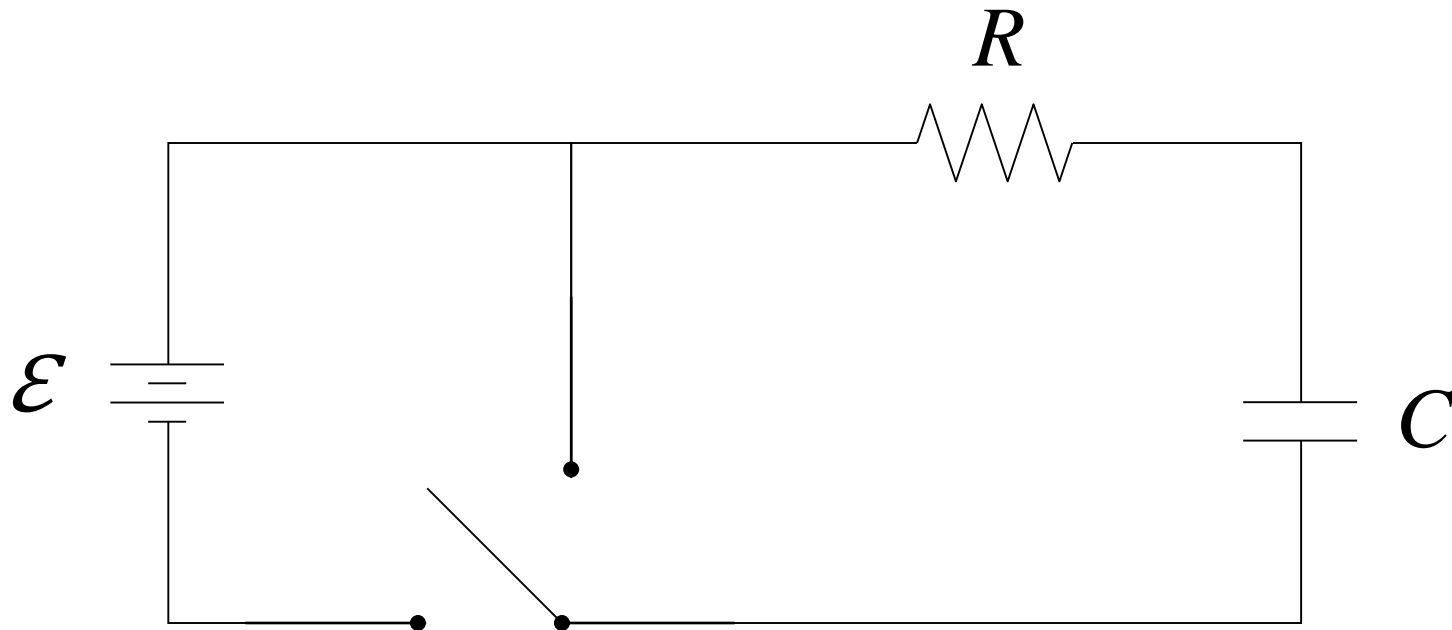
The capacitor in the circuit below is charged and discharged using the SPDT switch. Find expressions for voltage and current as functions of time.



## Behavior of basic $RC$ Circuit: Charging


- The loop equation  $\mathcal{E} - IR - q/C = 0$  becomes the differential equation  $\mathcal{E} - (dq/dt)R - q/C = 0$ .
- The solution for  $q(t)$  is an inverse exponential function with the time constant  $\tau = RC$  that “plateaus” with the capacitor reaching a full charge  $\mathcal{E}/C$ .
- The product of resistance and capacitance is an amount of time that governs the rate at which the capacitor will charge. A nearly full charge is achieved in about  $5\tau$ . A greater resistance and or a greater capacitance will cause a proportional increase in the time for charging to occur.
- As the charge and voltage of the capacitor are rising, the current is undergoing an exponential decrease with the same time constant  $\tau = RC$ .

# Voltage vs. Time – Charging Capacitor

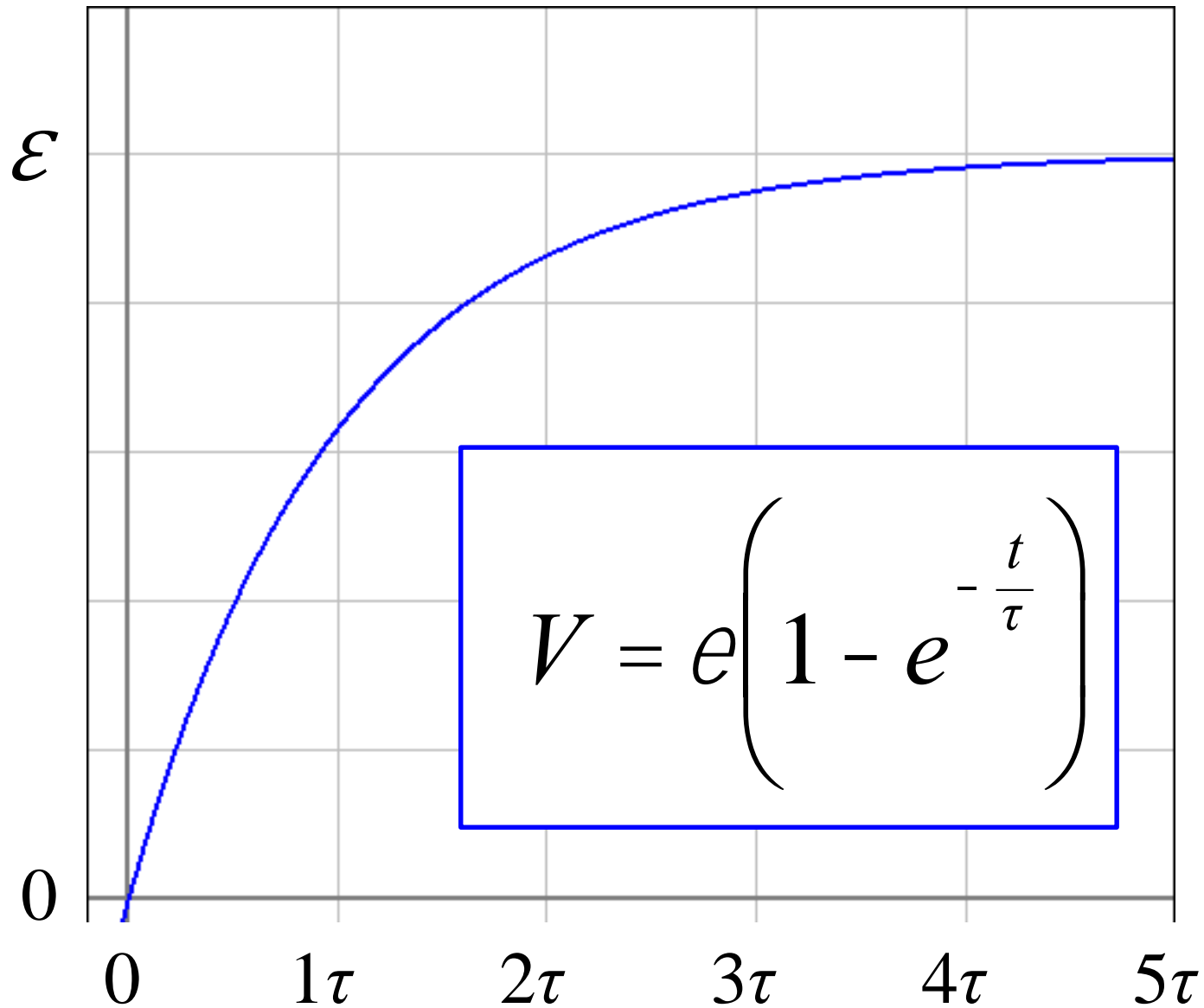

$\tau = RC$  (the “time constant”)

# Current vs. Time – Charging Capacitor

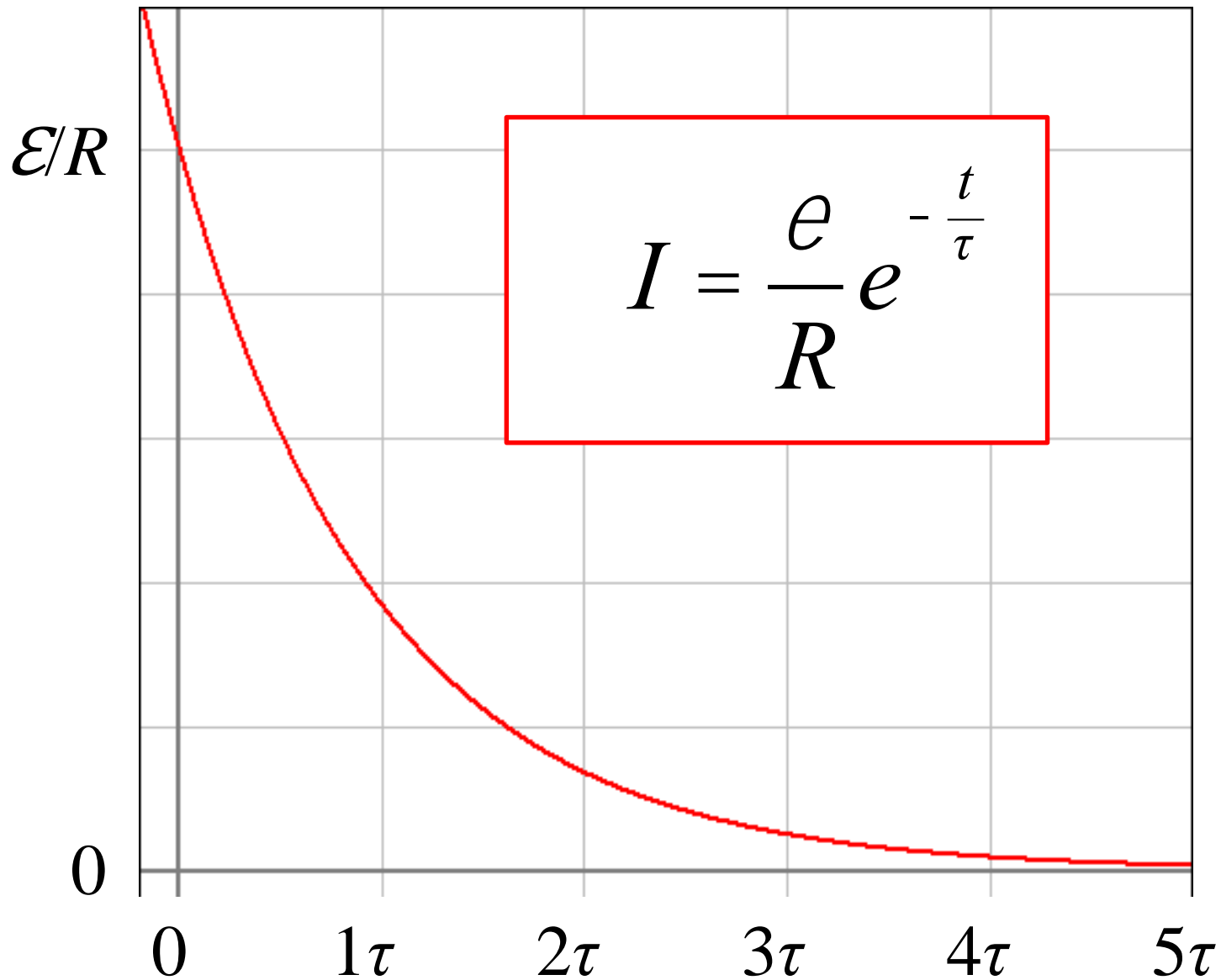

$\tau = RC$  (the “time constant”)




## Behavior basic $RC$ Circuit: Discharging

- The loop equation  $-IR - q/C = 0$  becomes the differential equation  $-(dq/dt)R - q/C = 0$ .
- The solution for  $q(t)$  is an exponential decay function with the time constant  $\tau = RC$  that drops to zero as the capacitor loses its charge.
- The product of resistance and capacitance is an amount of time that governs the rate at which the capacitor will charge. A near complete discharge occurs in about  $5\tau$ . A greater resistance and or a greater capacitance will cause a proportional increase in the time for discharging to occur.
- As the charge and voltage of the capacitor are falling, the current is also undergoing an exponential decrease with the same time constant  $\tau = RC$ .

## Charge or Voltage of a Capacitor

time	charging	discharging
0	0 %	100 %
$1\tau$	63 %	37 %
$2\tau$	86 %	14 %
$3\tau$	95 %	5 %
$4\tau$	98 %	2 %
$5\tau$	99 %	1 %


Current (A)

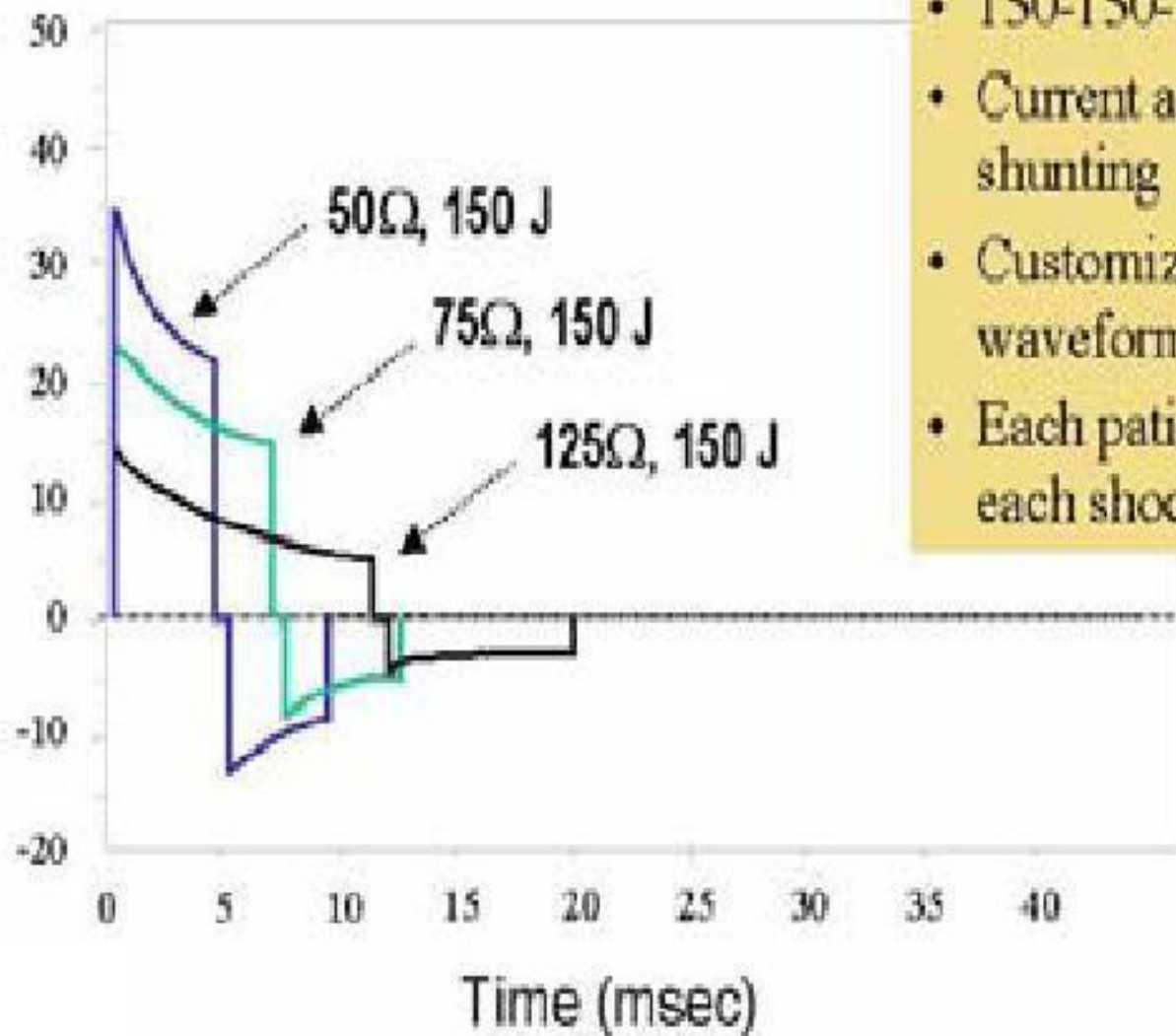

- 150-150-150 J
- Current adjusted for shunting
- Customized waveform shape
- Each patient and each shock


$C = 100 \mu\text{F}$

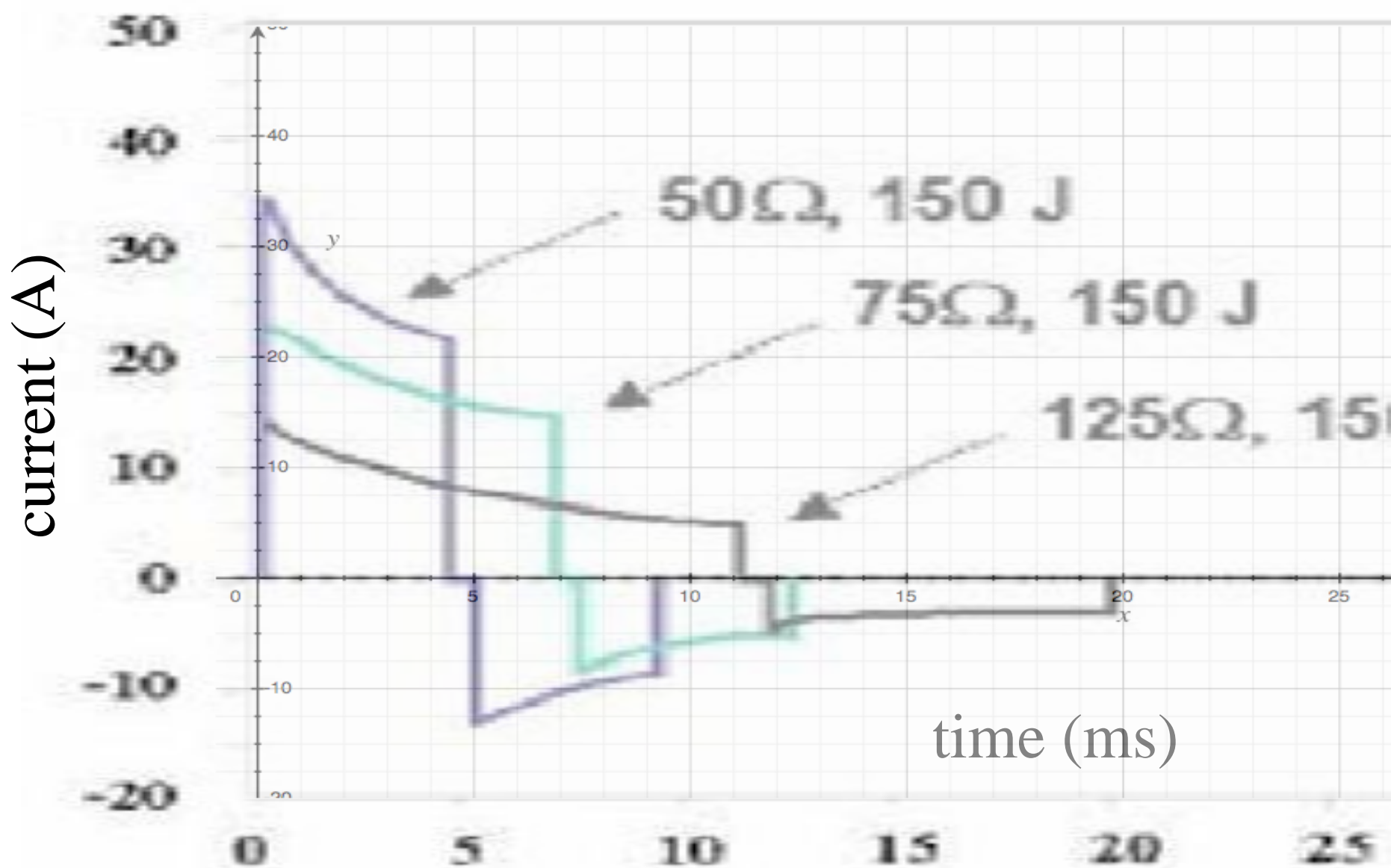This is information for a defibrillator – essentially an  $RC$  circuit!  
The resistance is that of the patient's chest between the two paddles that are used to deliver the shock as the capacitor discharges.



Use the information on the graph to determine the capacitance and compare to published value.


# Mini-Lab: Time a Capacitor Discharge

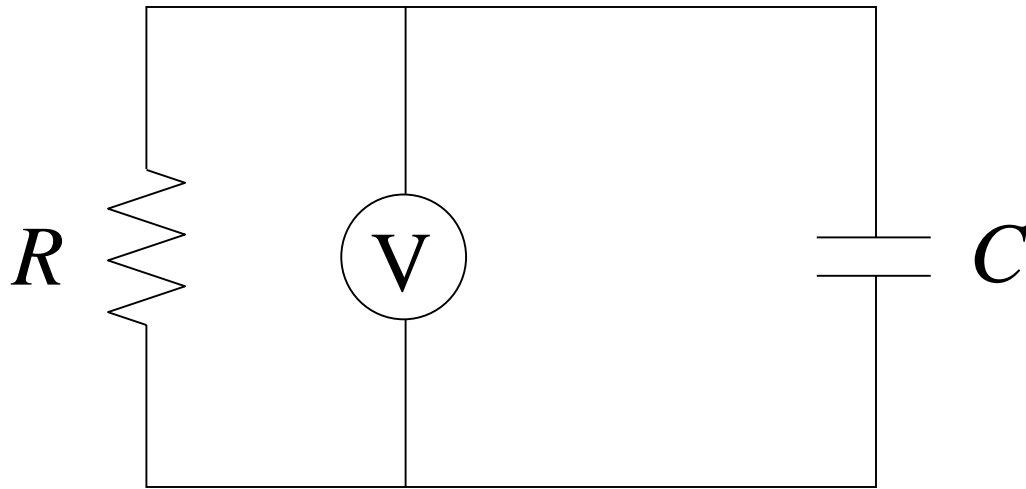

Collect data using a stopwatch. Use the “Lap” button to pause and unpaue the total elapsed time displayed. The capacitor has been previously charged by a 6 V battery and will begin to discharge as soon as the circuit is completed.

Voltage (V)	Time (s)
4.00	0.00
3.00	
2.00	
1.00	
0.50	

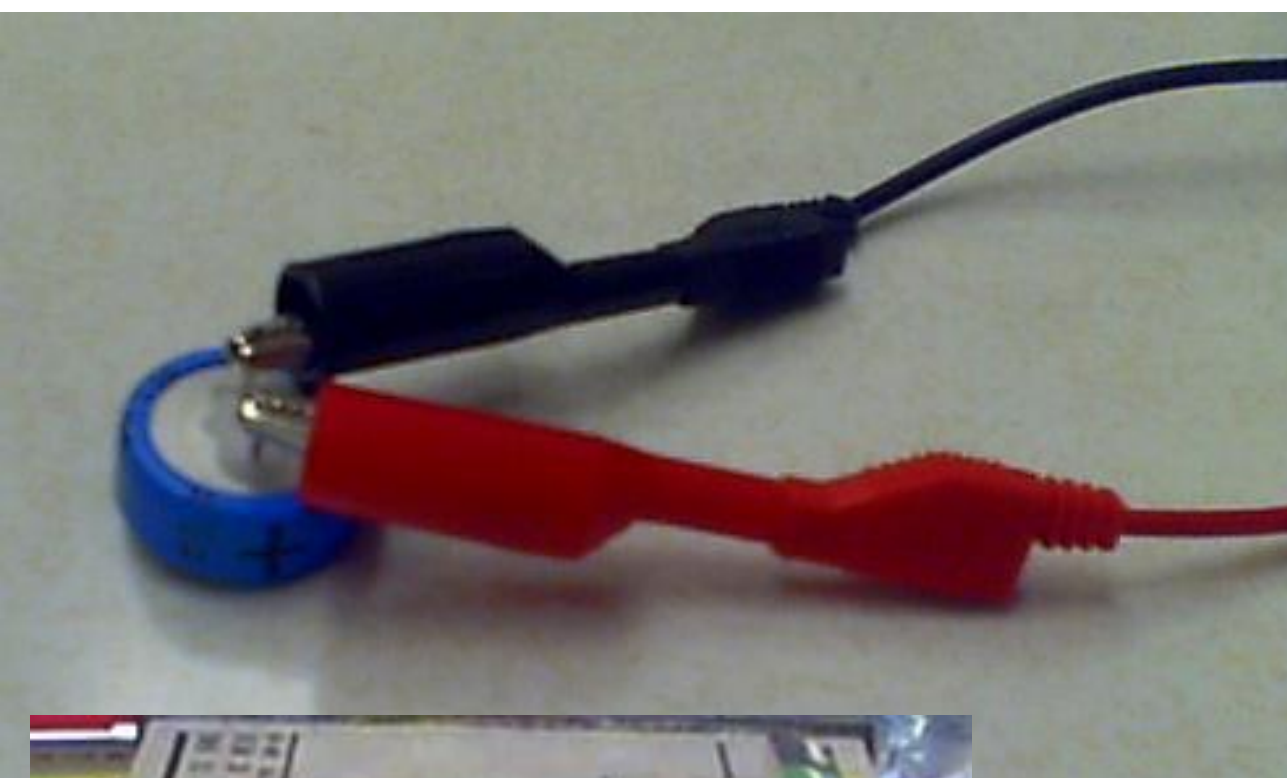For convenience let  $t = 0$  be the point in time when the capacitor reaches 4 volts as it discharges.




Notice the  
polarity of the  
capacitor!

Do **NOT** yet  
connect!



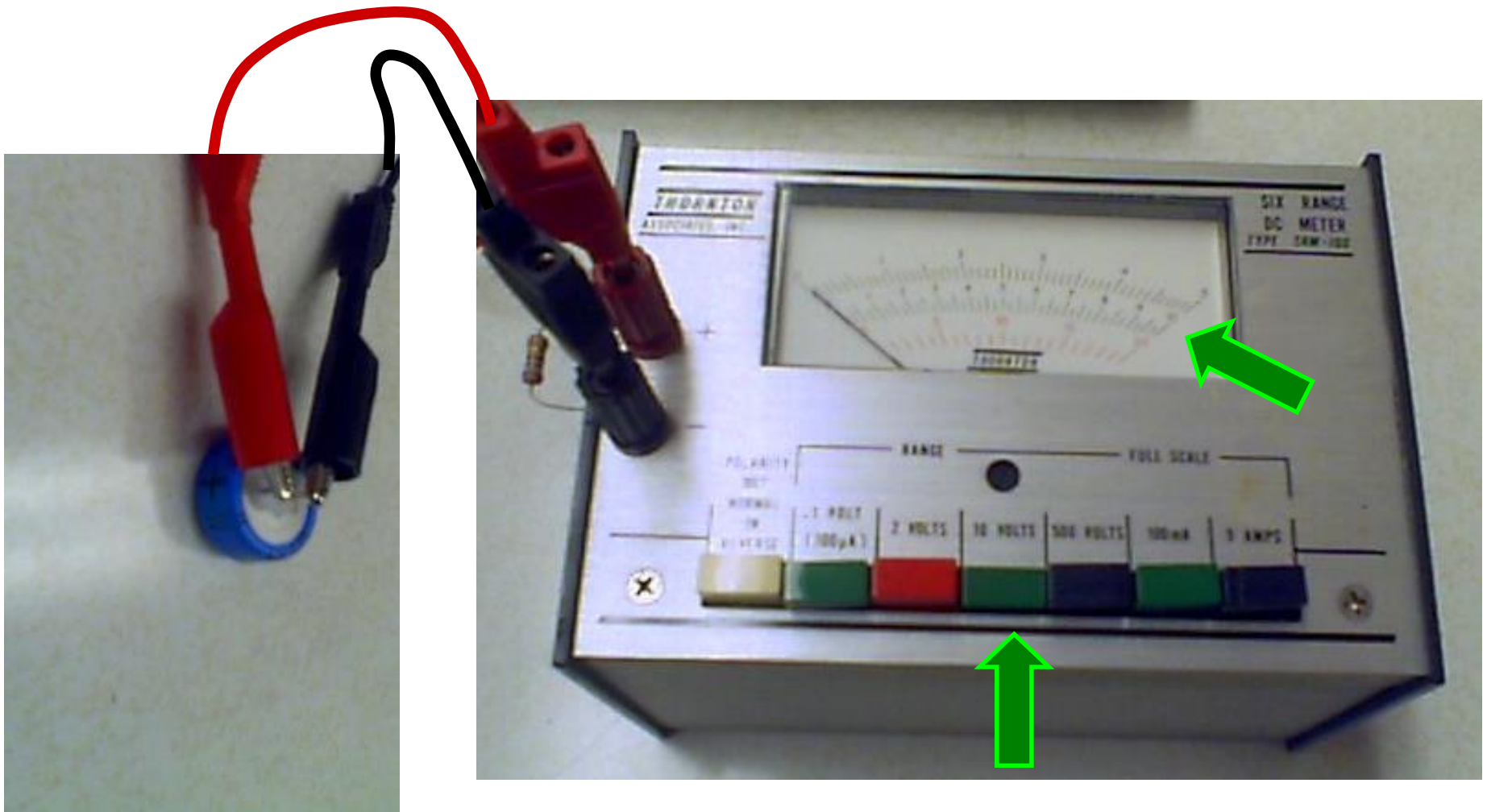*Gently* connect the  
resistor to the  
terminals of the meter  
– tighten *very little!*




Do **NOT** connect until you are *ready to time* with stopwatch!

Use the 10 volts scale.

Voltage (V)	Time (s)
4.00	0.00
3.00	14.55
2.00	42.02
1.00	94.70
0.50	154.98

 1. How much time does it take for the voltage to halve? Use this time and the value of  $R$  to solve for  $C$ .
2. Plot the data and perform an exponential regression.
3. Use the regression equation to determine the time constant and use to find  $C$ .




```

EDIT [ ] TESTS
7: QuartReg
8: LinReg(a+bx)
9: LnReg
8 ExpReg
H: PwrReg
B: Logistic
C: SinReg

```




# Voltage vs. Time for 1 F Capacitor

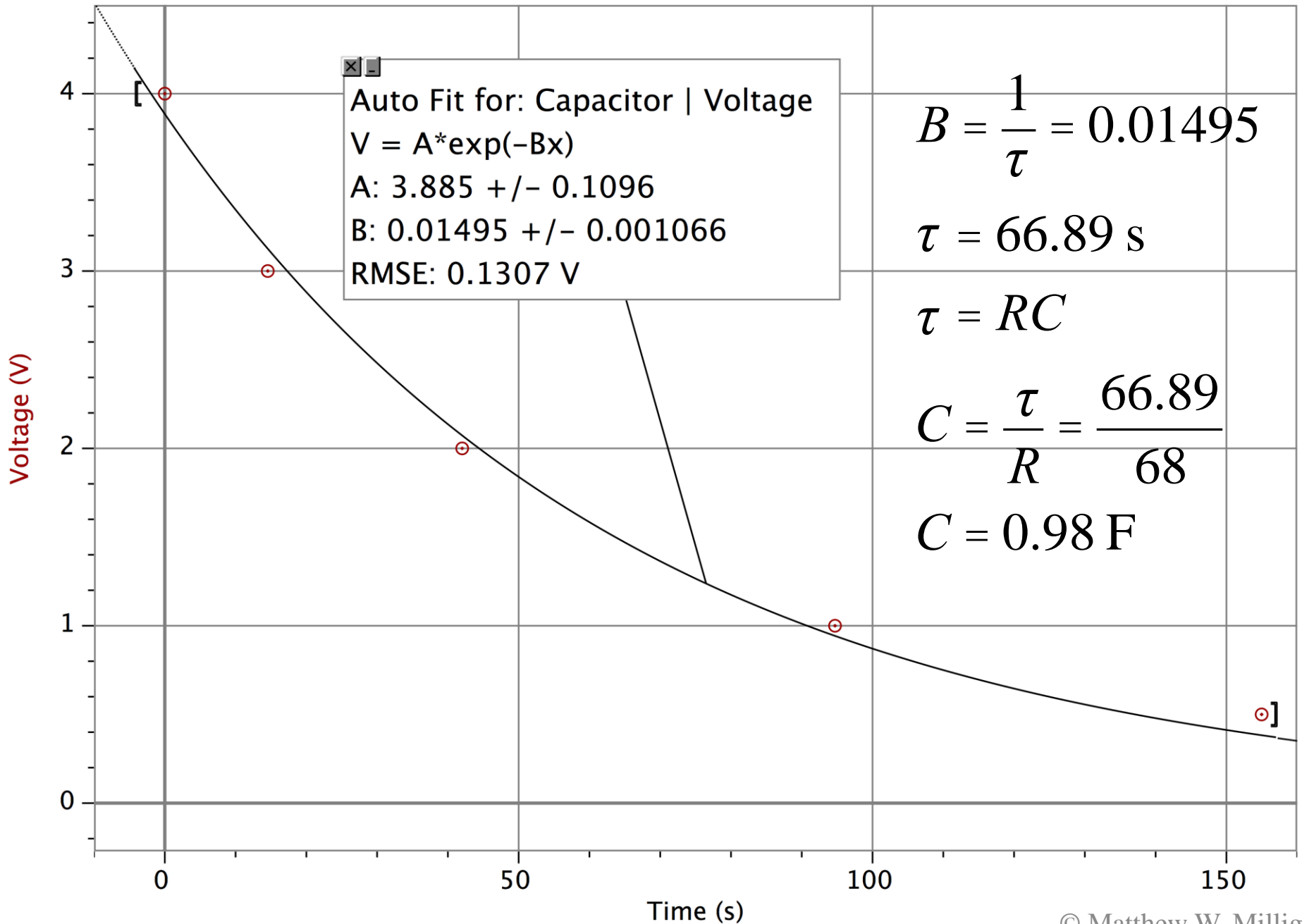


Voltage (V)	Time (s)	$\ln(V)$	$\ln(V/V_0)$
4.00	0.00	1.386	0.000
3.00	14.55	1.099	-0.288
2.00	42.02	0.693	-0.693
1.00	94.70	0.000	-1.386
0.50	154.98	-0.693	-2.079

An alternate way to analyze exponential data is to use logarithms...


# Natural Log Voltage vs. Time

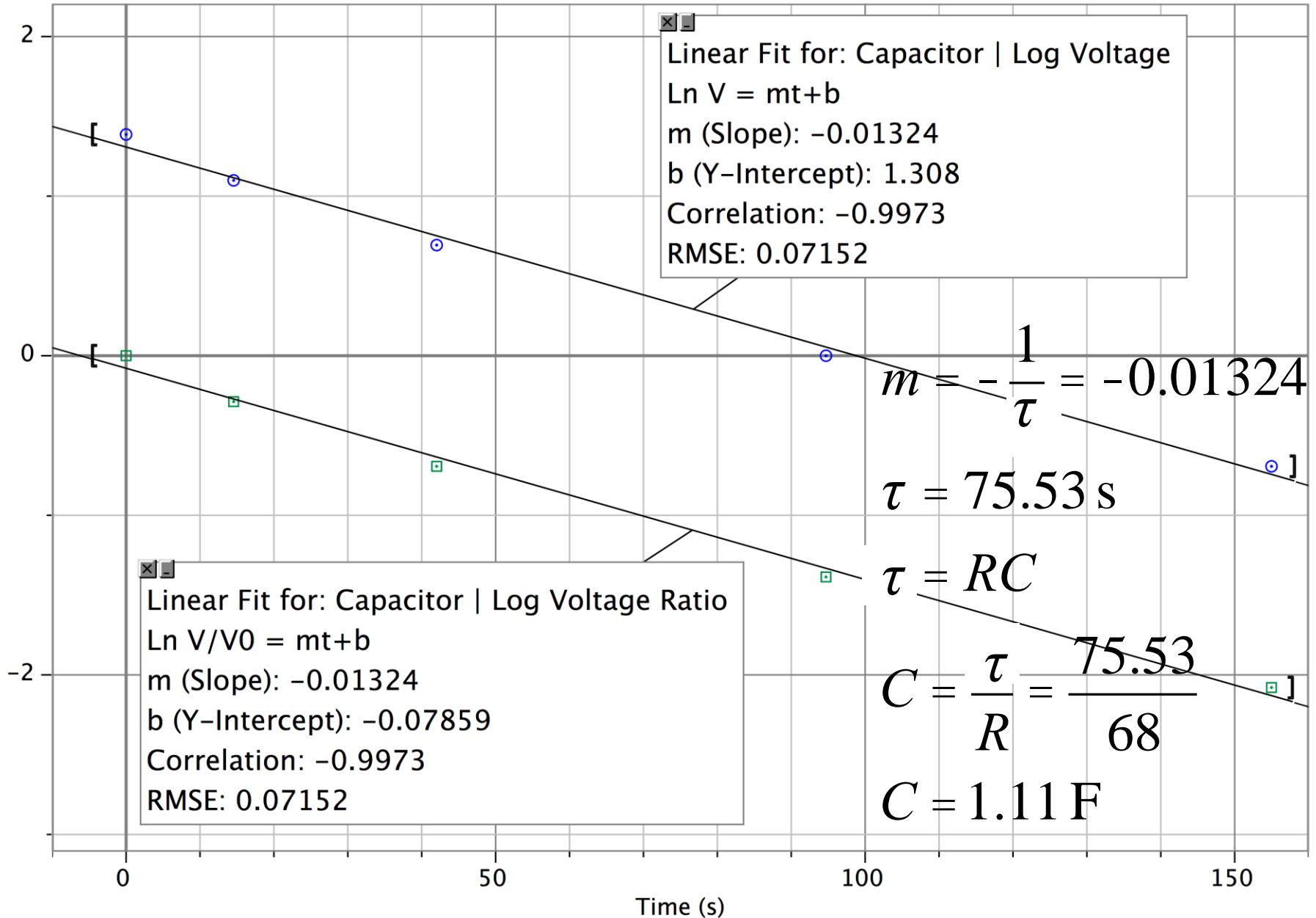

# Voltage vs. Time (logarithmic scale)

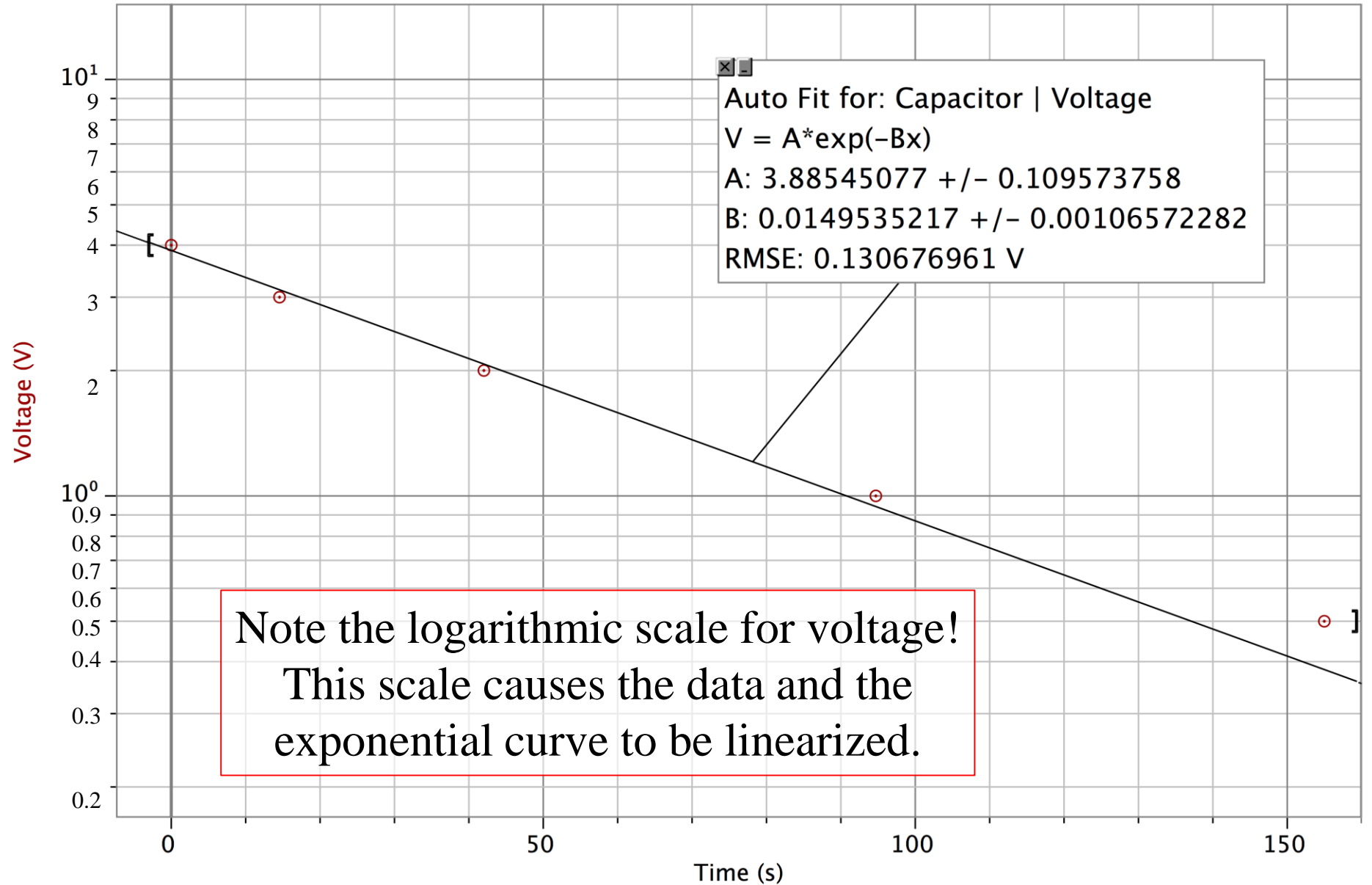


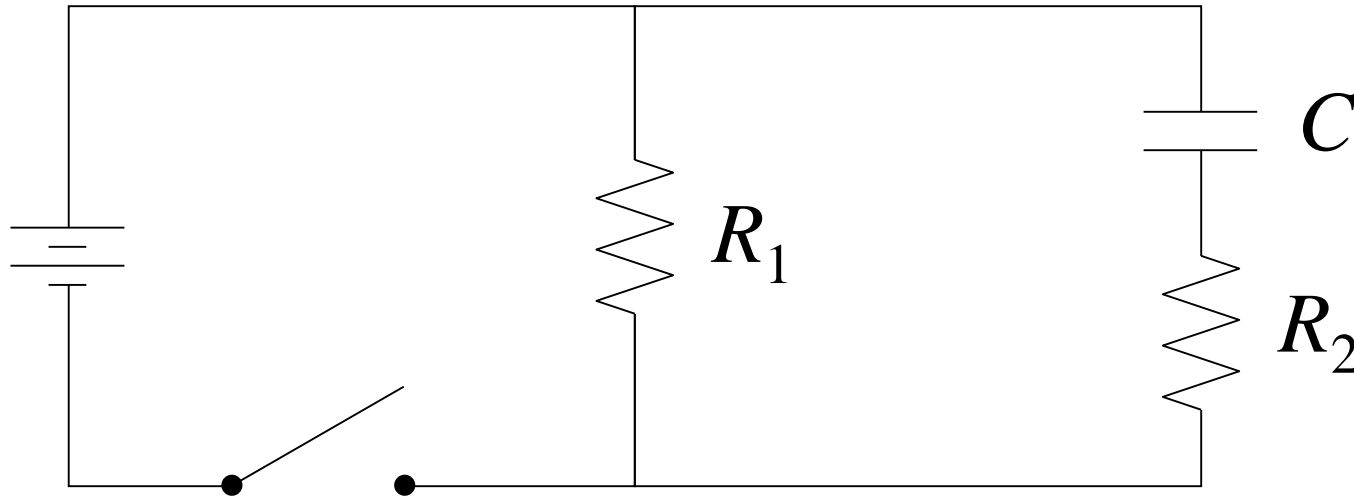Resistors  $R_1 = 330 \, \Omega$ ,  $R_2 = 470 \, \Omega$ , capacitor  $C = 2.2 \, \text{mF}$ , and a 1.50 V battery are connected as shown. The switch is closed at  $t = 0$  and then opened at  $t = 100.0 \, \text{s}$ . (a) Find the times at which the voltage of the capacitor is 0.75 V. (b) Make a careful sketch of current vs. time for the battery and for  $R_2$ .




In principle any and every capacitor circuit problem can be solved by writing Kirchoff node and loop equations, substituting  $I = dq/dt$ , and solving the system of differential equations. However, there is often an easier way using only the notion of the time constant  $\tau = RC$  and appropriate exponential functions... (go to the next page to see)

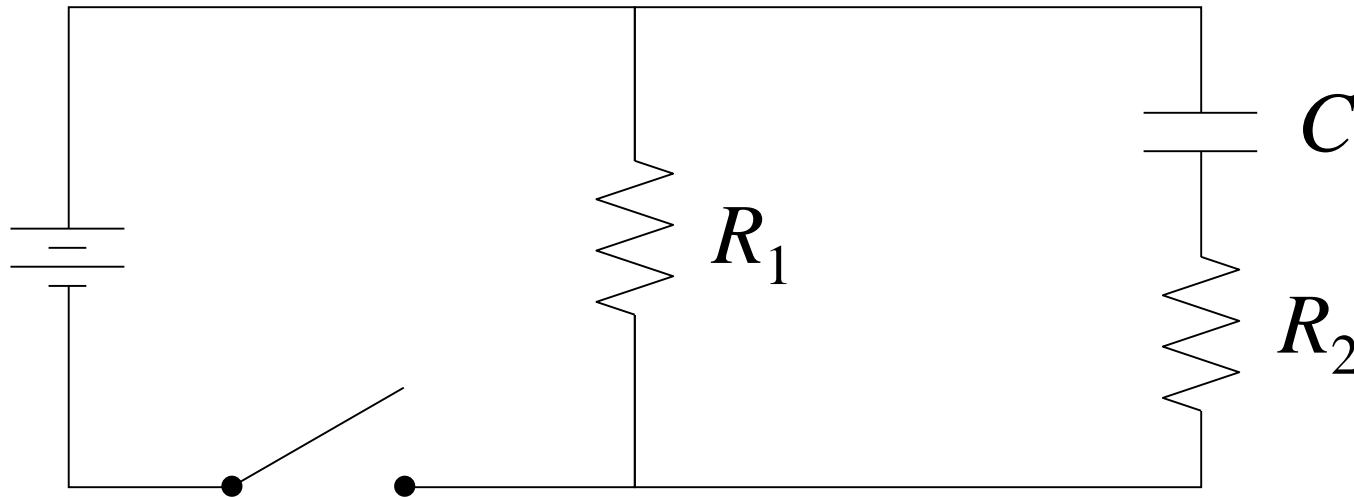Resistors  $R_1 = 330 \, \Omega$ ,  $R_2 = 470 \, \Omega$ , capacitor  $C = 2.2 \, \text{mF}$ , and a 1.50 V battery are connected as shown. The switch is closed at  $t = 0$  and then opened at  $t = 100.0 \, \text{s}$ . (a) Find the times at which the voltage of the capacitor is 0.75 V. (b) Make a careful sketch of current vs. time for the battery and for  $R_2$ .



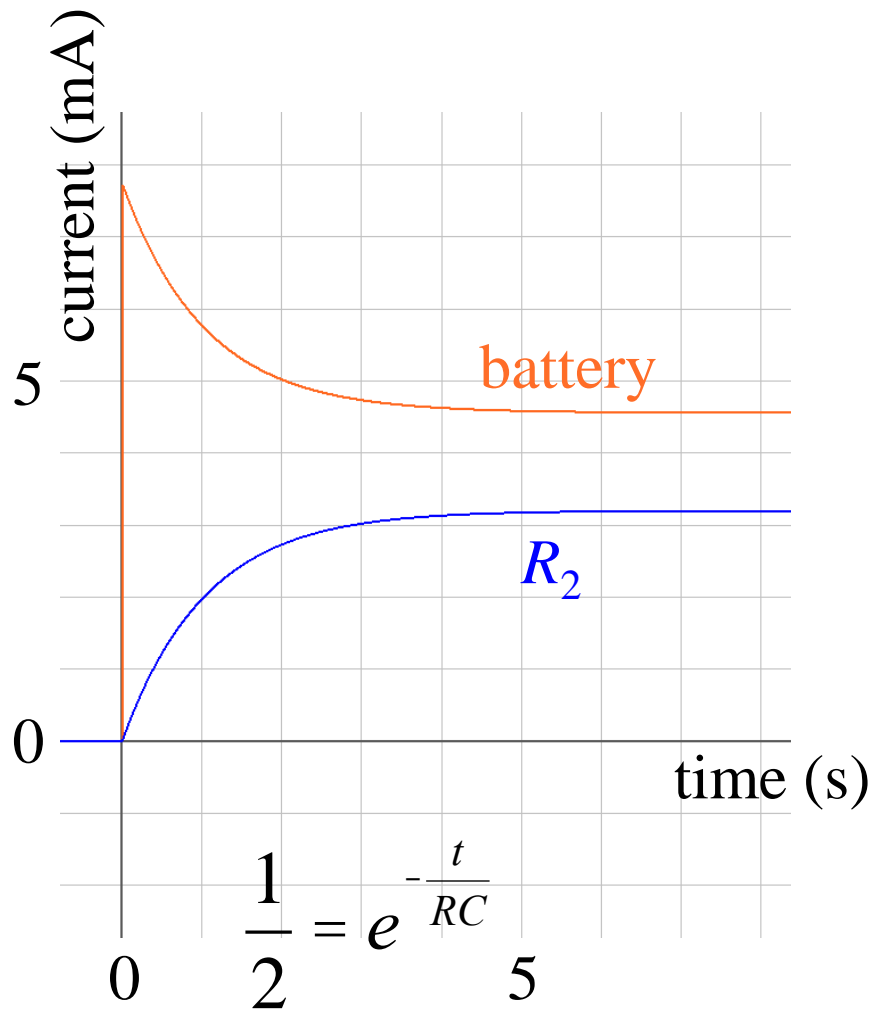Many circuits are like this – solve by comparison to the “basic  $RC$  circuit”. When the switch closes the time constant will be  $R_2C$  ( $R_1$  does not affect the charging of the capacitor). And when the switch opens the time constant will be  $(R_1 + R_2)C$ . All that remains is to apply logical exponential functions using these time constants...



$$\frac{1}{2} = e^{-\frac{t}{RC}}$$

$$t = R_2 C \ln 2$$

$$t = 1.034 \ln 2$$

$$t = 0.717 \text{ s}$$


$$\frac{1}{2} = e^{-\frac{Dt}{RC}}$$

$$Dt = (R_1 + R_2) C \ln 2$$

$$Dt = 1.76 \ln 2$$


$$Dt = 1.22 \text{ s}$$

$$t = 101.22 \text{ s}$$

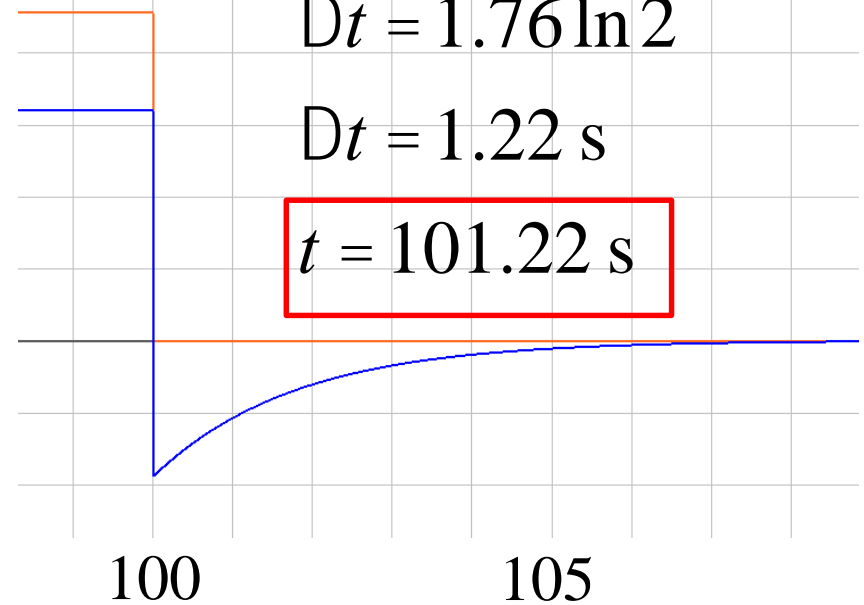

The two times when the voltage of the capacitor is 0.75 volts.

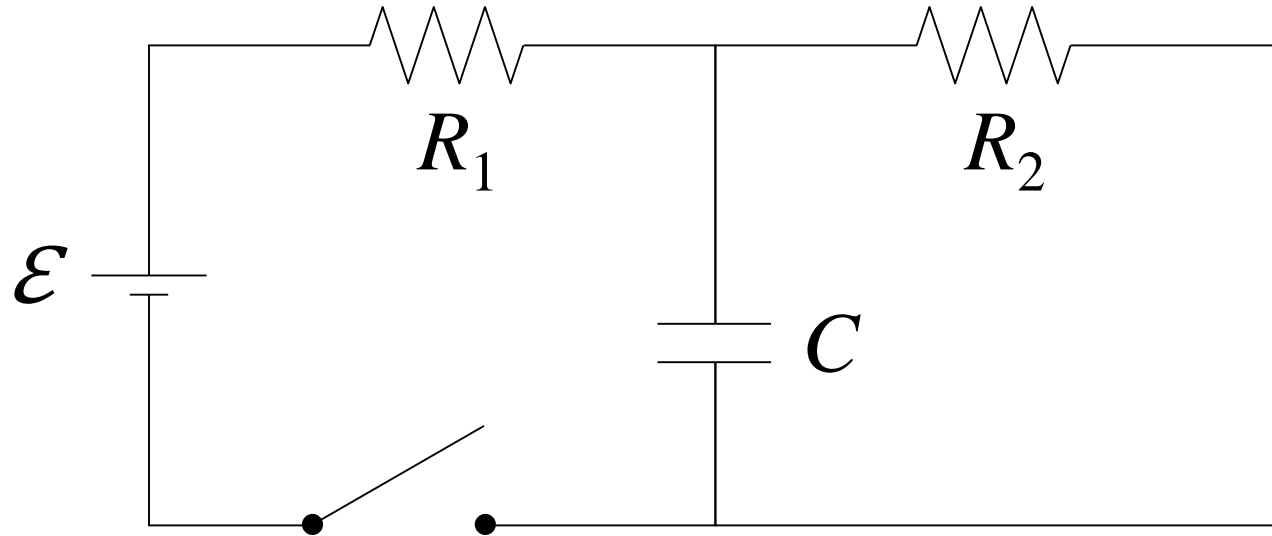
The capacitor in the circuit below is charged and discharged by closing and opening the switch. (a) Sketch voltage vs. time graphs for each resistor and the capacitor. Find the time constant for (b) discharging and (c) charging.



When the switch opens the time constant is  $R_2C$  as discharging occurs. However when the switch closes it is not obvious what happens! Sometimes it may be necessary to apply node and loop differential equations! It can be shown for this particular circuit that the time constant will be given by  $\tau = R_1R_2C/(R_1 + R_2)$  as charging occurs.



supposing  $R_1 > R_2$

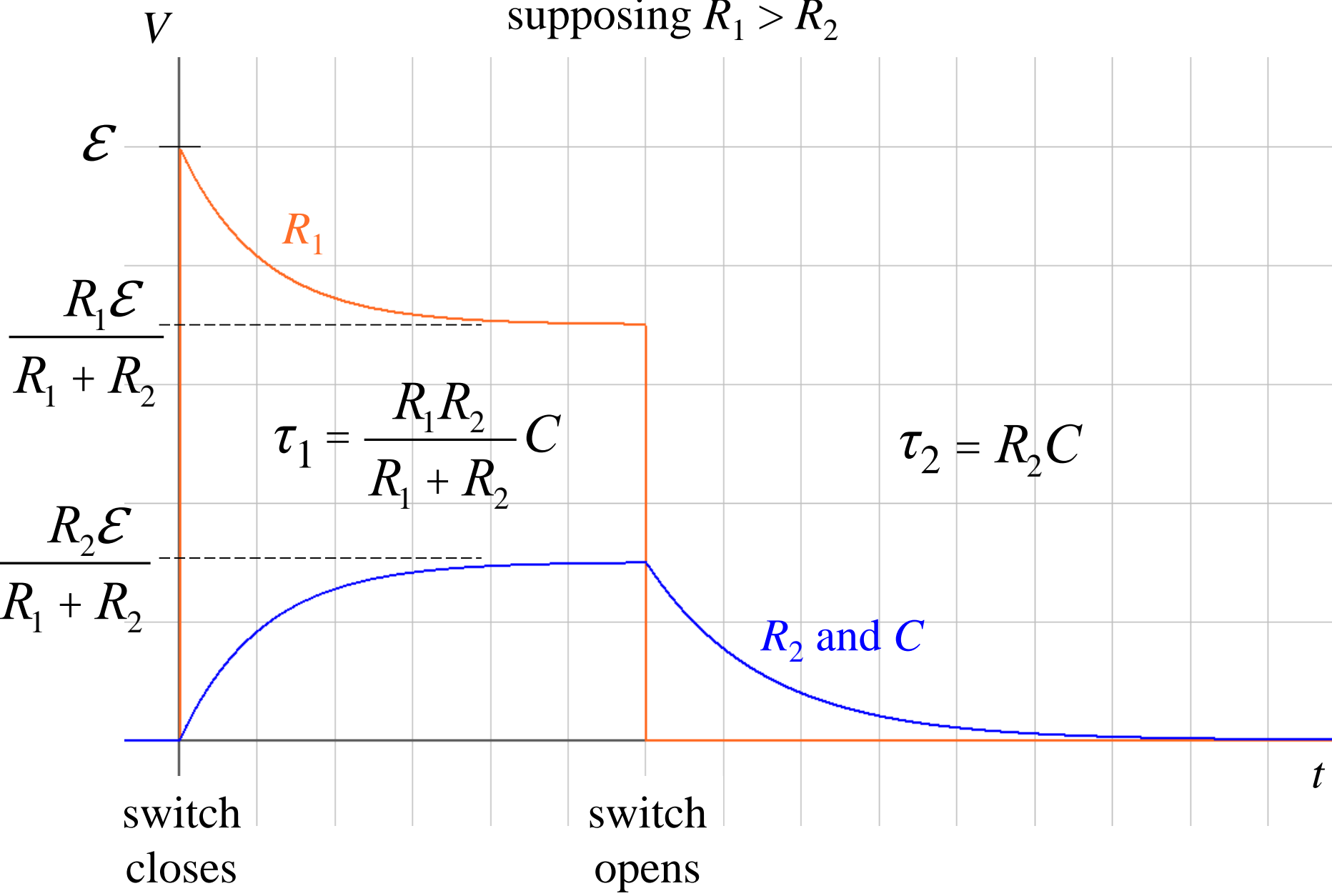

supposing  $R_2 > R_1$

