


Electrical Circuits

- I. Current and Resistance
 - Ohm's Law
- II. Resistivity
 - resistance factors
 - conductivity
 - drift velocity & current density
- III. Electrical Power
- IV. Circuits
 - series and parallel
 - Kirchoff's Laws
- V. Batteries and Meters**
 - internal resistance**

	The student will be able to:	HW:
1	Define current and the ampere, conventional positive current flow, and solve related problems, including those with both positive and negative charge carriers. ✓	1 – 3
2	Define resistance and the ohm, state Ohm's Law, and solve related problems involving ohmic and/or nonohmic devices. ✓	4 – 7
3	Describe and explain factors influencing resistance, state mathematical relation between resistance, length, area, and resistivity or conductivity, and solve related problems. ✓	8 – 13
4	Solve problems involving current density, electric field, resistivity, drift velocity and/or use these concepts to explain the nature of resistance. ✓	14 – 16
5	Solve problems involving electric power. ✓	17 – 21
6	Determine effective resistance of a network of series and/or parallel resistors. ✓	22 – 24
7	Solve for voltage, current, resistance, and power in DC circuits using Kirchoff's Laws and/or effective resistance. ✓	25 – 38
8	Model a cell or battery as an ideal voltage source or as an EMF with internal resistance and a certain terminal voltage, and solve related problems.	39 – 43
9	Understand operation and properties of voltmeters and ammeters and illustrate proper connections thereof, and solve related problems.	44 – 46

Cells & Batteries

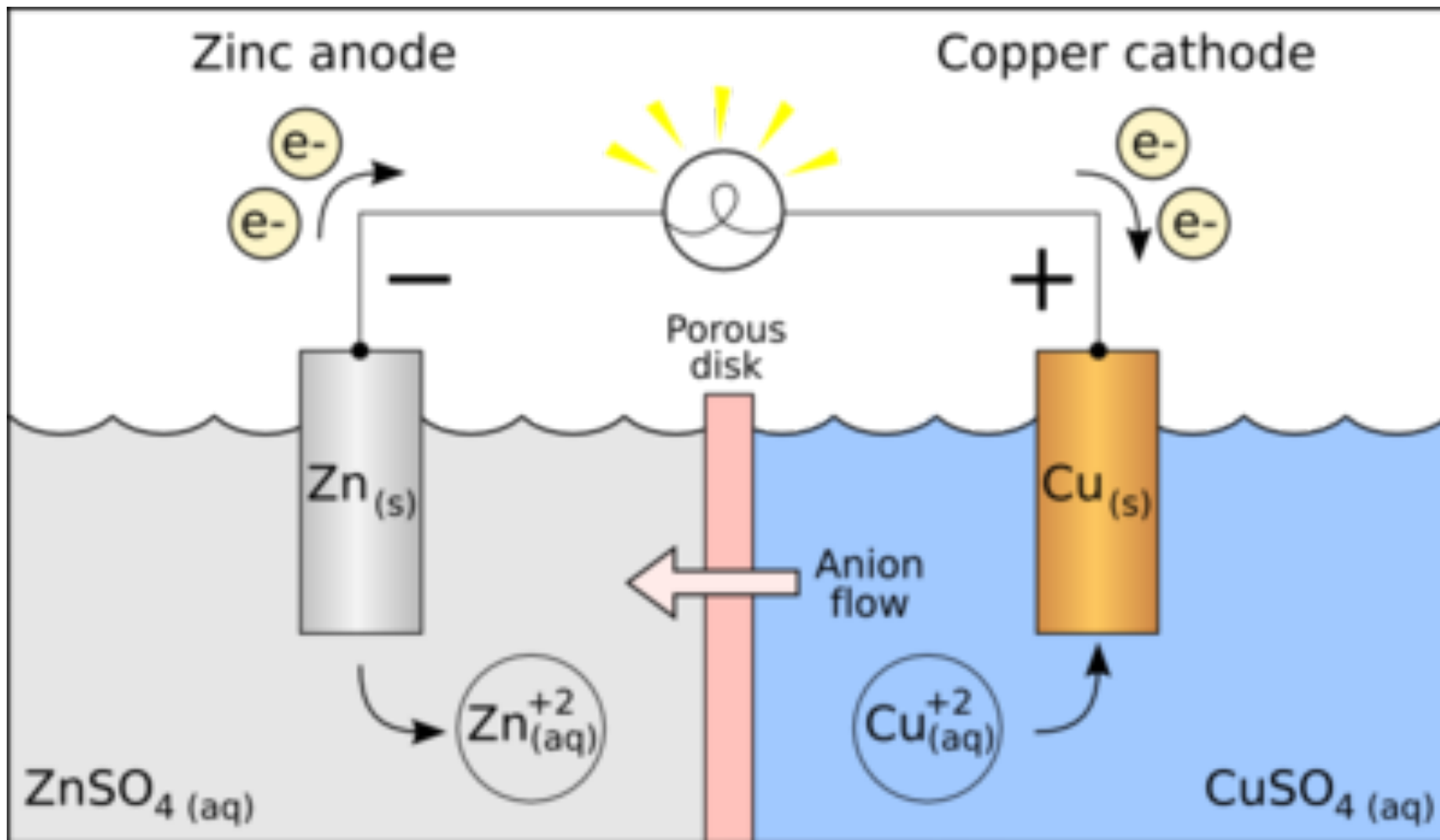
- A voltaic (or galvanic) cell is a single container of chemicals with two electrodes: an anode and a cathode.
- Properly speaking a “battery” is a collection of multiple cells connected in series.
- Energy is “stored” in chemical form until a current is drawn from the battery, at which point oxidation occurs at the anode and reduction occurs at the cathode.



source: Wikipedia, Ohiostandard

EMF

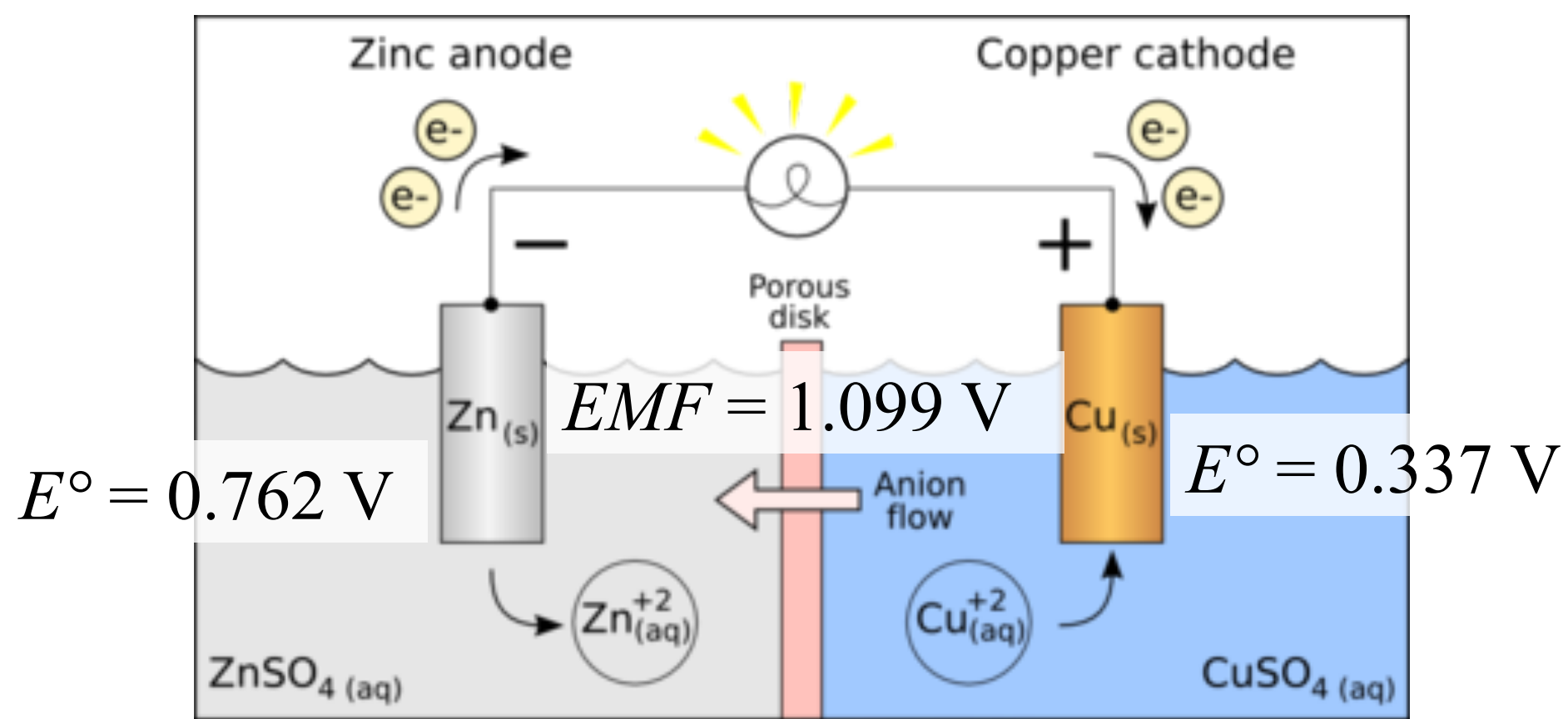- The energy associated with the chemical reaction can be quantified by *EMF* (“electromotive force”), which is a measure of energy per charge.
- For a given chemical reaction there is a characteristic *EMF*, which is independent of the quantity of reactants and can be determined by standard electric potentials of the corresponding half-reactions.



source: Wikipedia, Ohiostandard

The potential or *EMF* (electromotive force) is the combination of the half-potentials of the reactions.


For this particular combination of reactions:

$$EMF = 0.762 + 0.337 = 1.099 \text{ V}$$

Terminal Voltage and Internal Resistance

- A battery's voltage has a *tendency* to be *relatively constant*. However it is the EMF of the chemical reaction that should be constant.
- The voltage measured at the terminals of the battery is variable depending on the current. The greater the current leaving the positive terminal, the less the terminal voltage.
- The variance in terminal voltage is a result of internal resistance associated with the flow of charge through the battery.

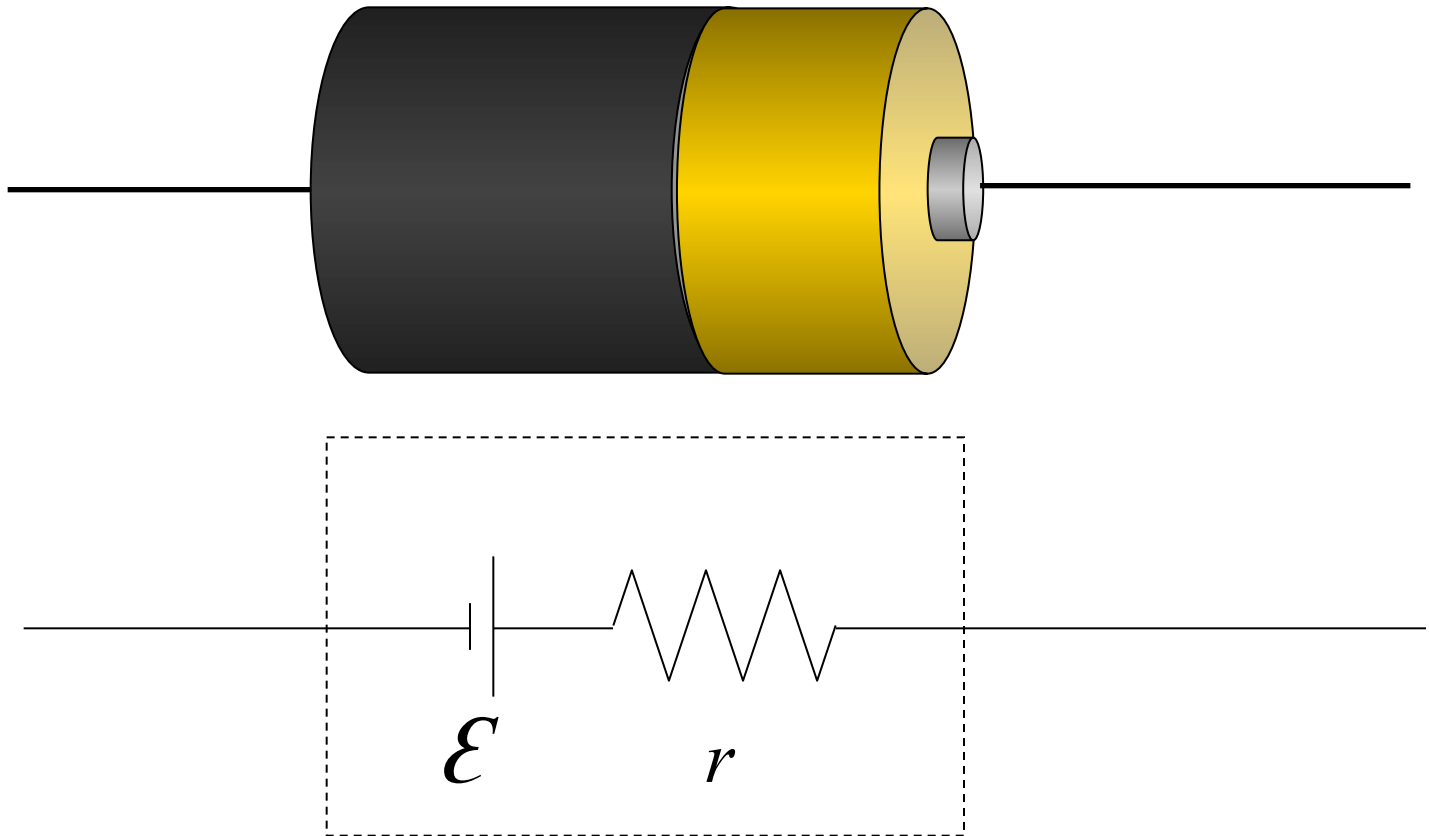
Modeling the Behavior of a Cell or Battery



where: $\mathcal{E} = \text{emf}$

$r = \text{internal resistance}$

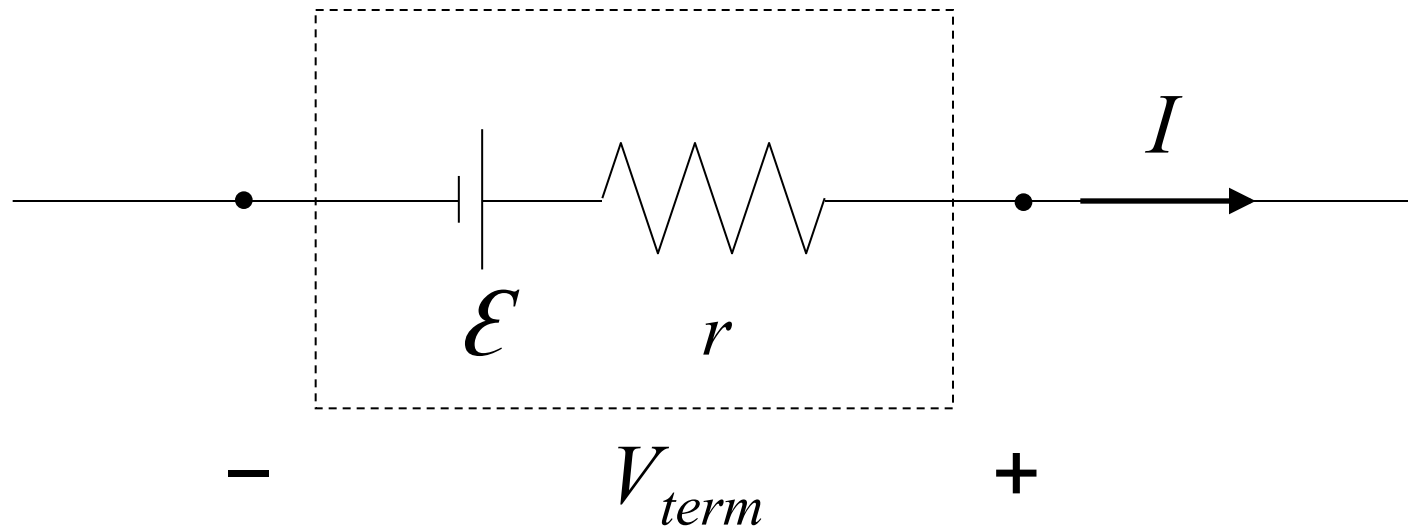Modeling the Behavior of a Cell or Battery



Note: in spite of the commonly used schematic of this model there is not an actual resistor inside a battery. The resistor symbol shown here represents the resistance that “occurs” throughout the battery as charge passes from one terminal to the other.

$$V_{term} = \mathcal{E} - Ir$$

Electrical Circuits

- I. Current and Resistance
 - Ohm's Law
- II. Resistivity
 - resistance factors
 - conductivity
 - drift velocity & current density
- III. Electrical Power
- IV. Circuits
 - series and parallel
 - Kirchoff's Laws
- V. Batteries and Meters**
 - internal resistance**


	The student will be able to:	HW:
1	Define current and the ampere, conventional positive current flow, and solve related problems, including those with both positive and negative charge carriers. ✓	1 – 3
2	Define resistance and the ohm, state Ohm's Law, and solve related problems involving ohmic and/or nonohmic devices. ✓	4 – 7
3	Describe and explain factors influencing resistance, state mathematical relation between resistance, length, area, and resistivity or conductivity, and solve related problems. ✓	8 – 13
4	Solve problems involving current density, electric field, resistivity, drift velocity and/or use these concepts to explain the nature of resistance. ✓	14 – 16
5	Solve problems involving electric power. ✓	17 – 21
6	Determine effective resistance of a network of series and/or parallel resistors. ✓	22 – 24
7	Solve for voltage, current, resistance, and power in DC circuits using Kirchoff's Laws and/or effective resistance. ✓	25 – 38
8	Model a cell or battery as an ideal voltage source or as an EMF with internal resistance and a certain terminal voltage, and solve related problems. ✓	39 – 43
9	Understand operation and properties of voltmeters and ammeters and illustrate proper connections thereof, and solve related problems.	44 – 46

Electrical Meters

- When measuring a voltage or current it is inevitable that the circuit under consideration will be altered!
- It is useful to understand the properties of voltmeters and ammeters and their effect on a circuit...
- We will consider the “old school” technology of analog meters...



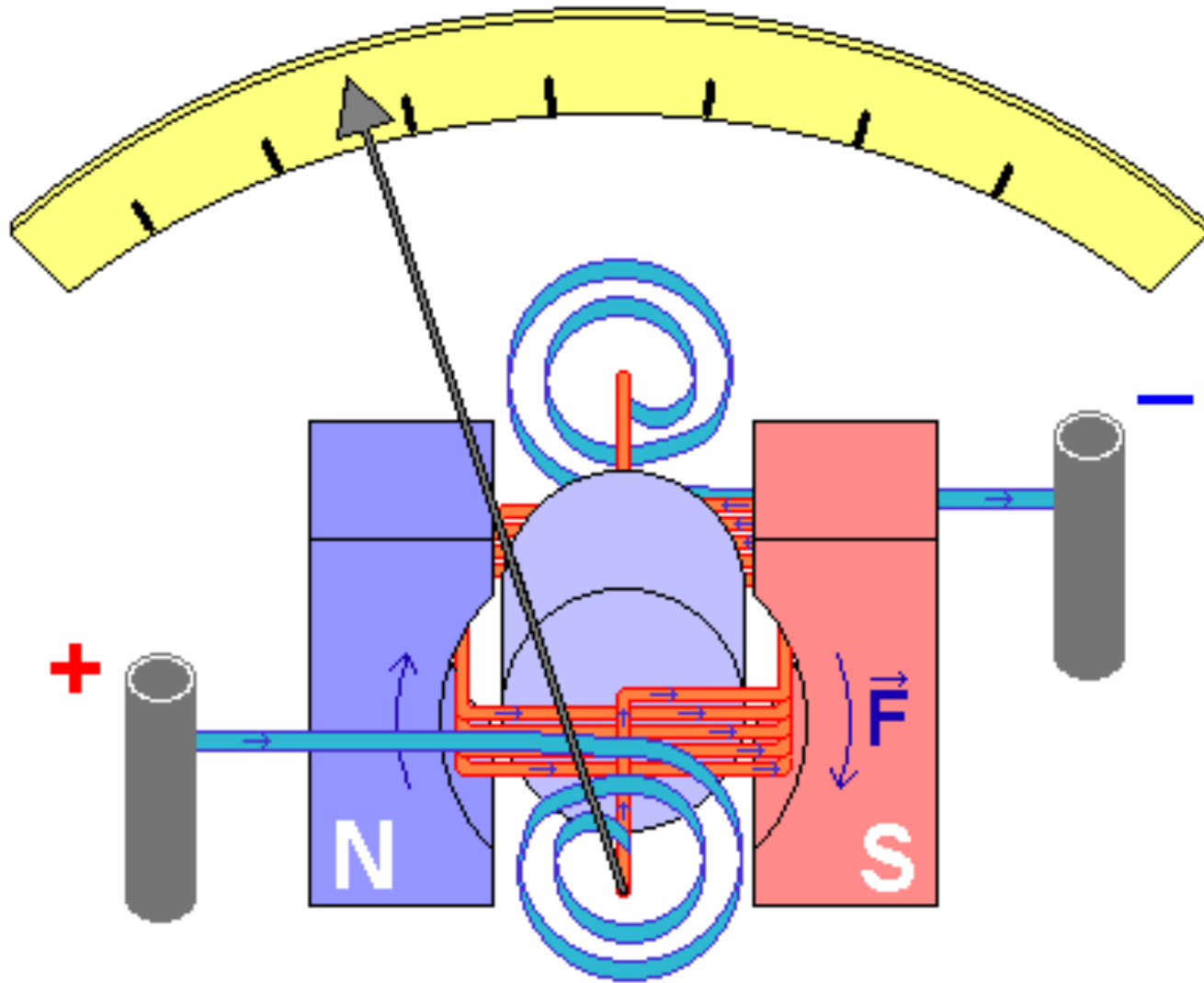Deflection of the needle is proportional to the current in the coil (interacts with permanent magnet).



Source: Wikipedia, Panther



A **galvanometer** is little more than the coil/needle/magnet apparatus. A relatively small current through the coil will cause the needle to deflect.




A **galvanometer** is characterized by its internal resistance (that of the coil) and its “full scale current” – enough to cause the needle to deflect to the end of the scale.

Voltmeter

- A **voltmeter** can be formed by connecting a galvanometer in series with a resistor.
- Typically a resistor of very large resistance is required to prevent overloading the coil.
- An “ideal voltmeter” would have *infinite* resistance and draw *zero* current. In reality an actual voltmeter has very large resistance and draws very little current.


Voltmeter Design

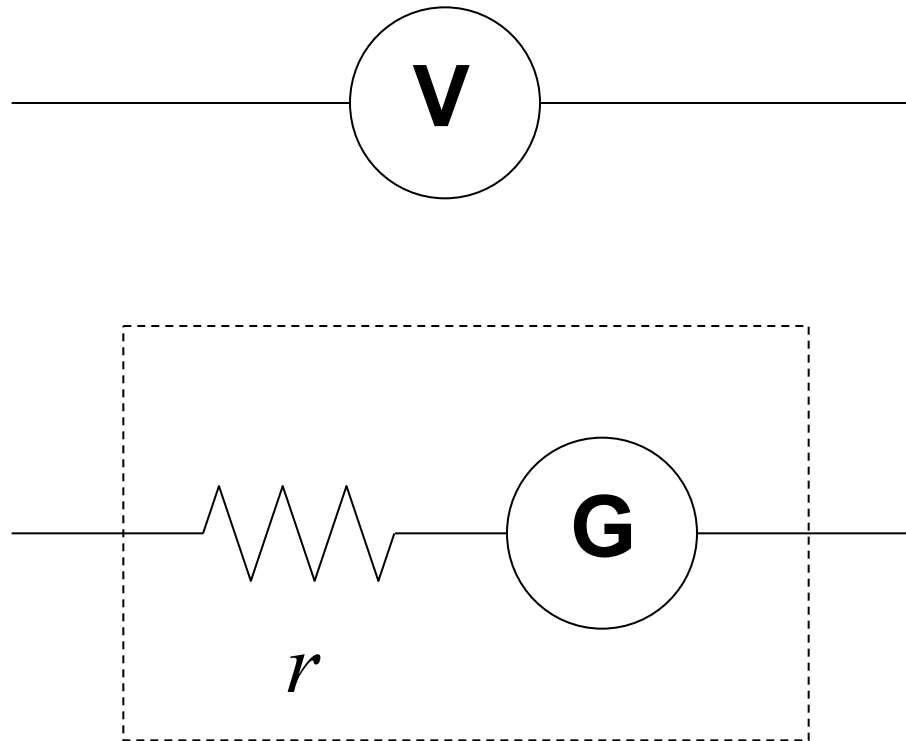

Ammeter

- An **ammeter** can be formed by connecting a galvanometer in parallel with a resistor.
- Typically the resistor must have very small resistance providing a “shunt” to prevent overloading the coil.
- An “ideal ammeter” would have *zero* resistance and not affect current. In reality an actual ammeter has very small resistance and may reduce current slightly.

Ammeter Design

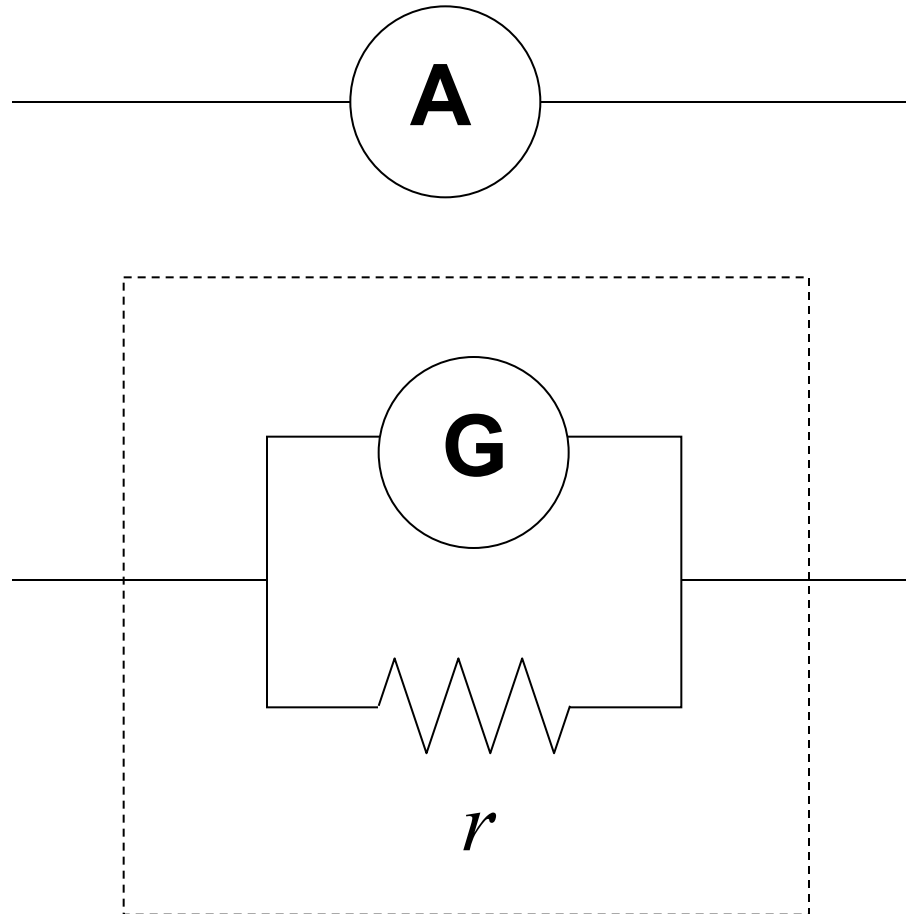


Multimeters




Analog



Digital

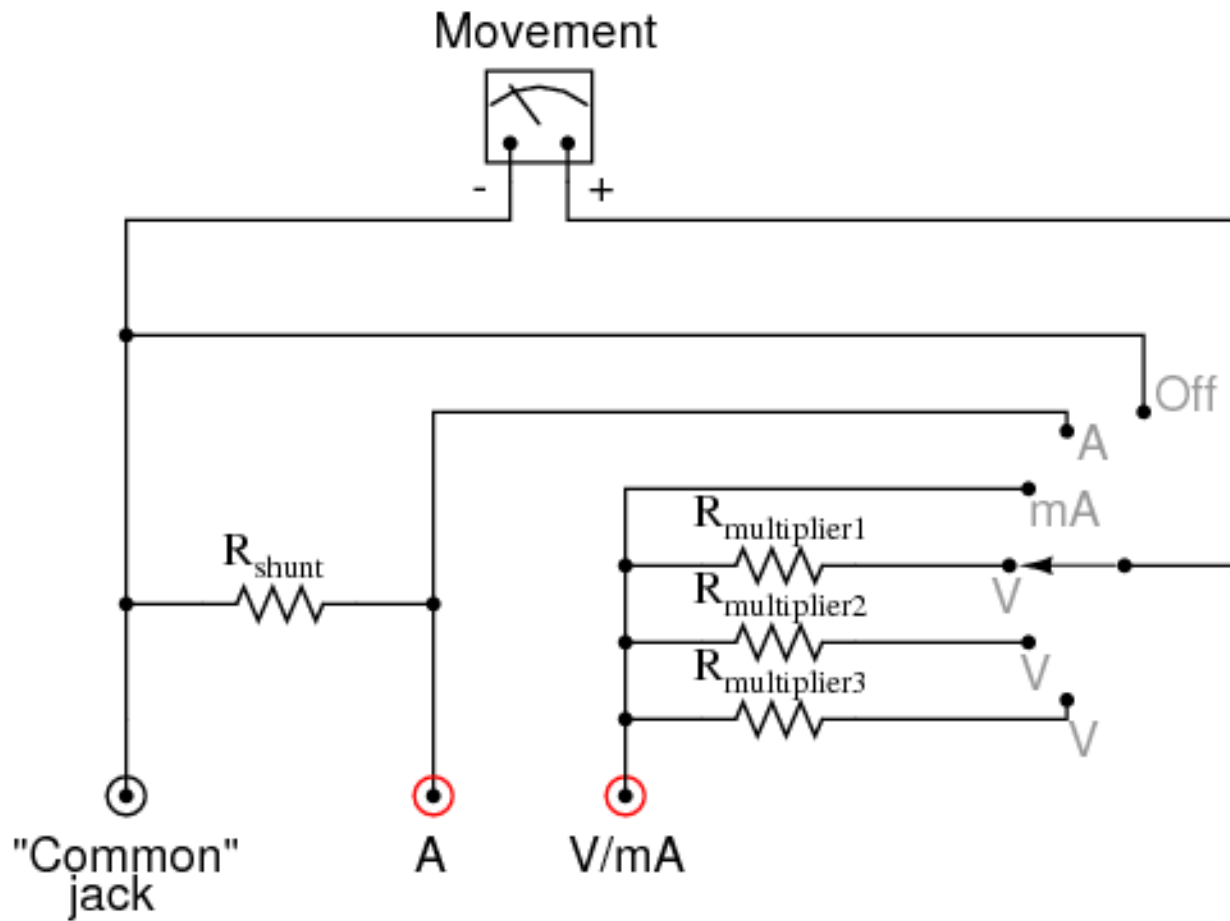

" $R_{\text{multiplier}}$ " resistors are actually rheostat networks

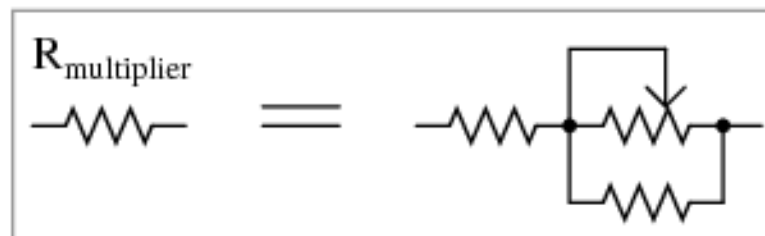




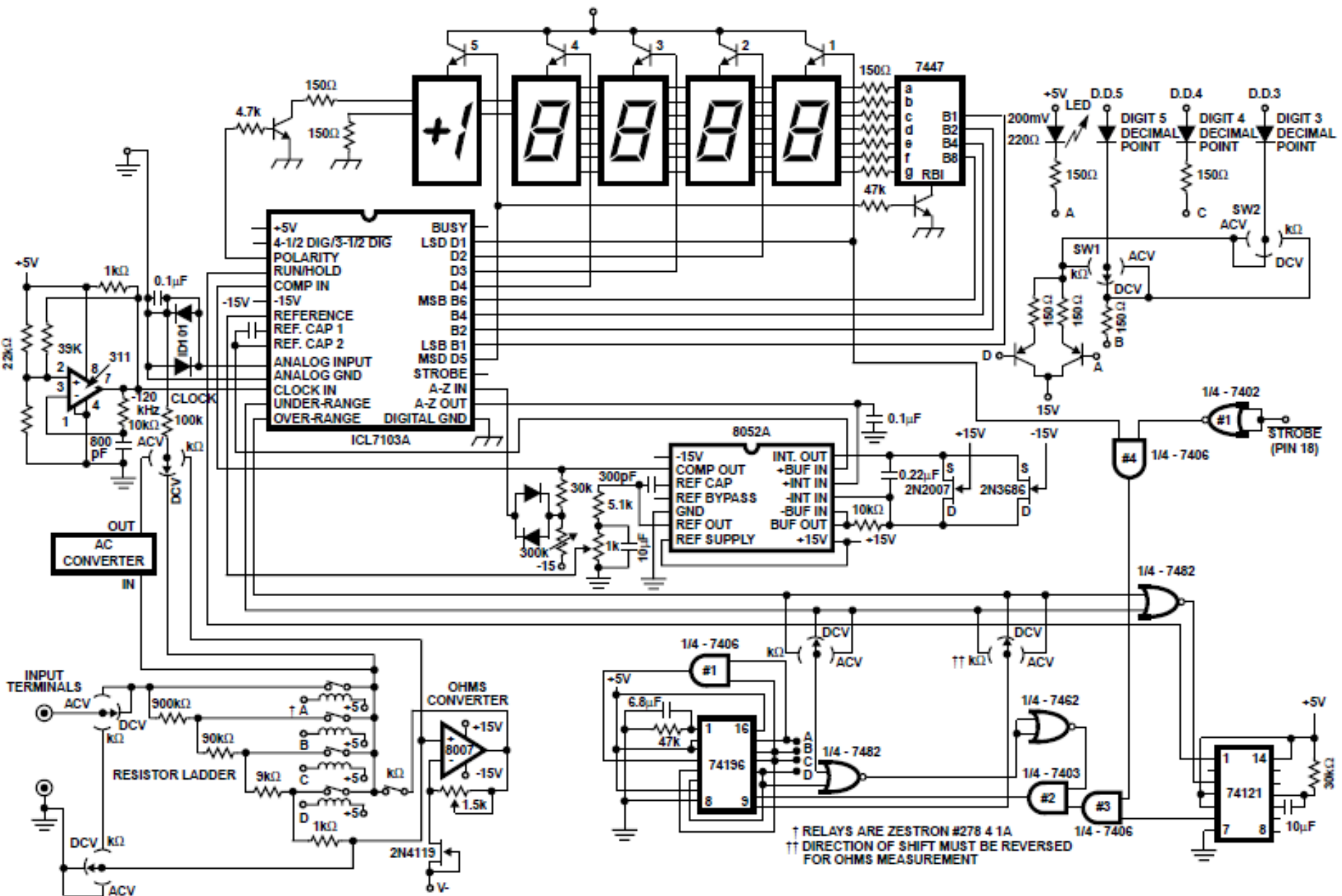


FIGURE 5. AUTO-RANGING SCHEMATIC #1

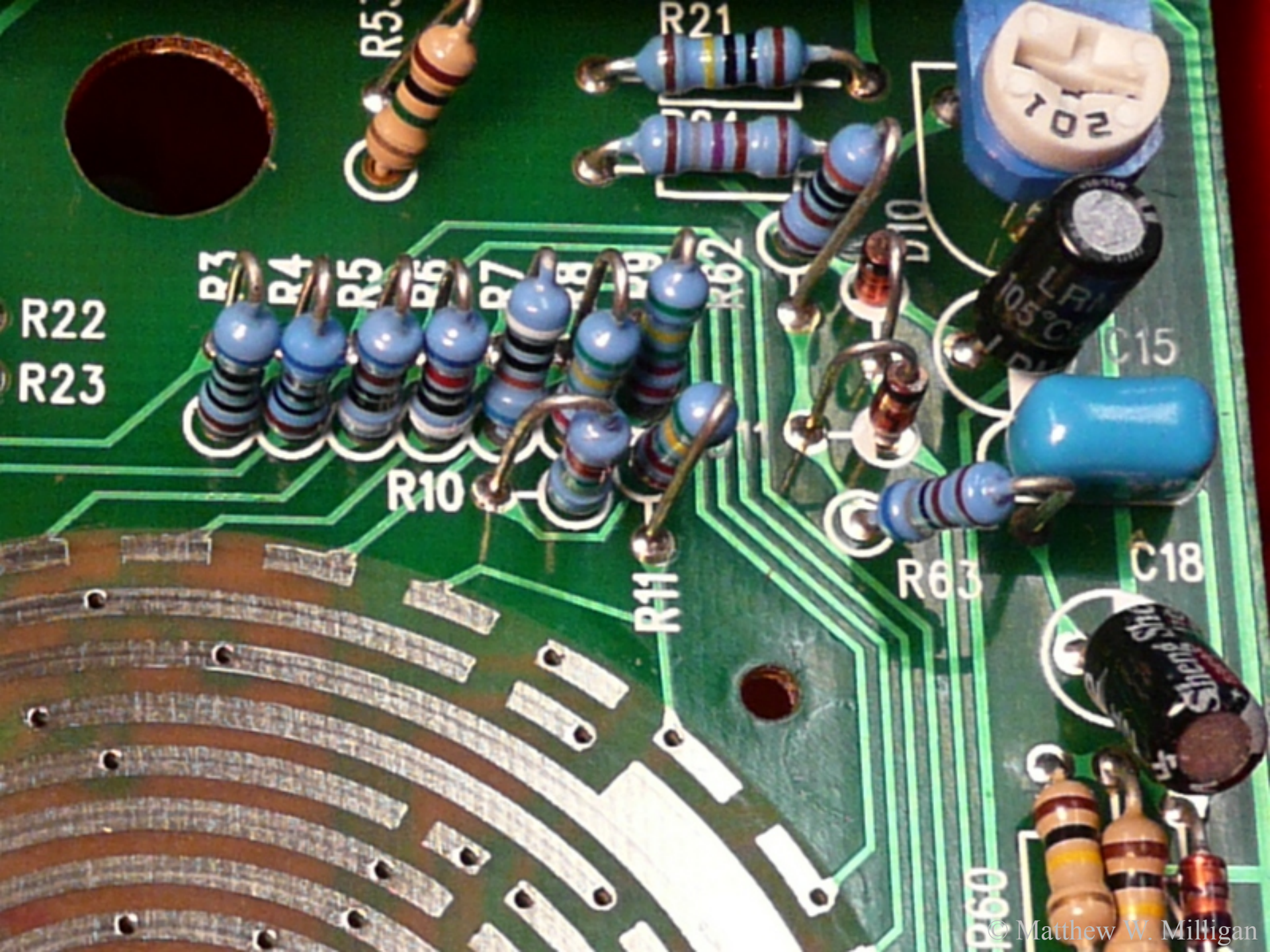

R22
R23

R3
R4
R5
R6
R7
R8
R9

R10

R11

R21

R62

R63

R5


D10

09p60

201
702

LF
105°C
C15

C18

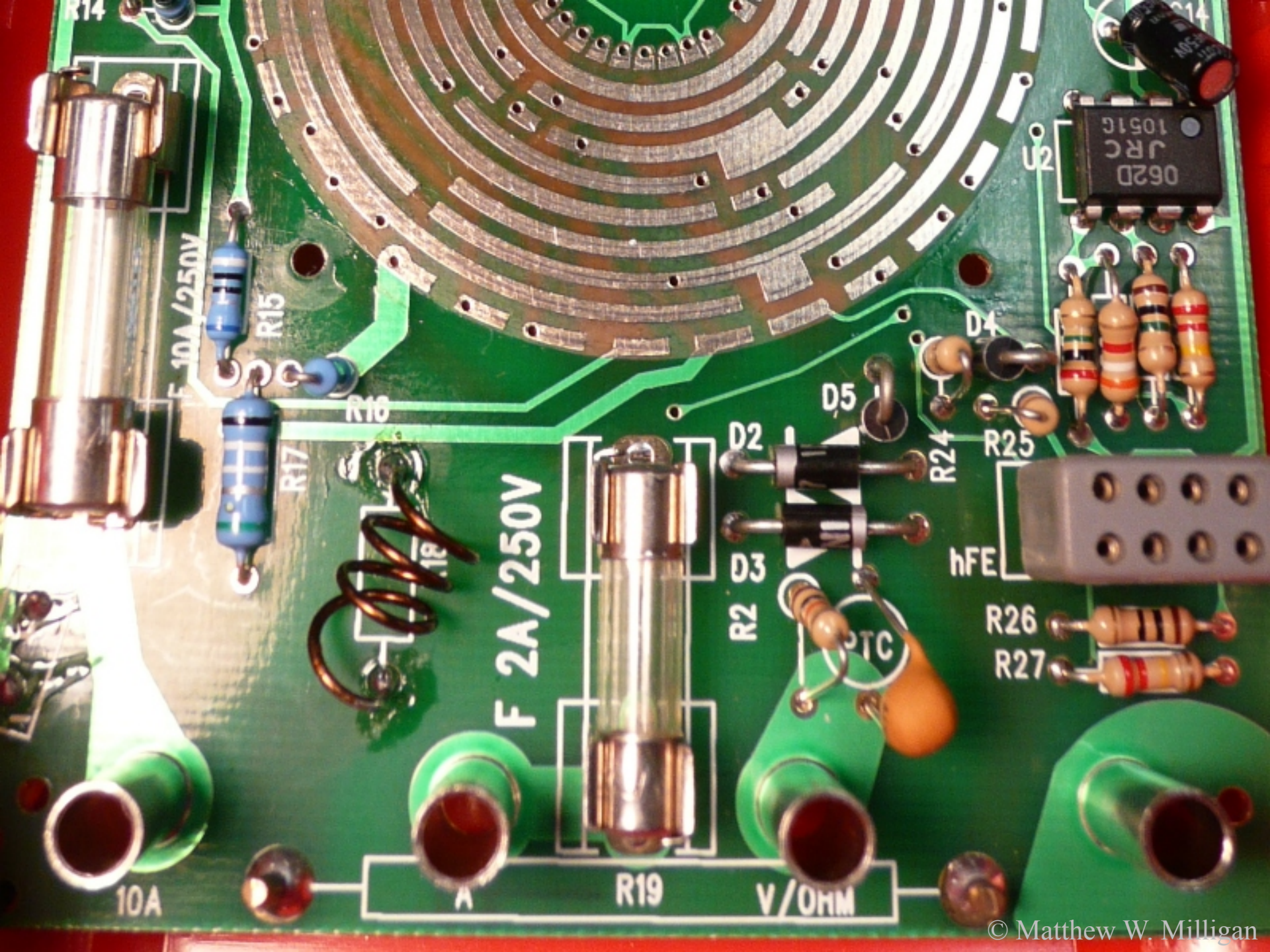

F 10A/250V

F 2A/250V

10A

A

R19

V/OHM

062D
JRC
1051C

hFE

R26

R27

D4

R24

R25

D5

D2

D3

R2


PTC

R15

R17

R16

U2

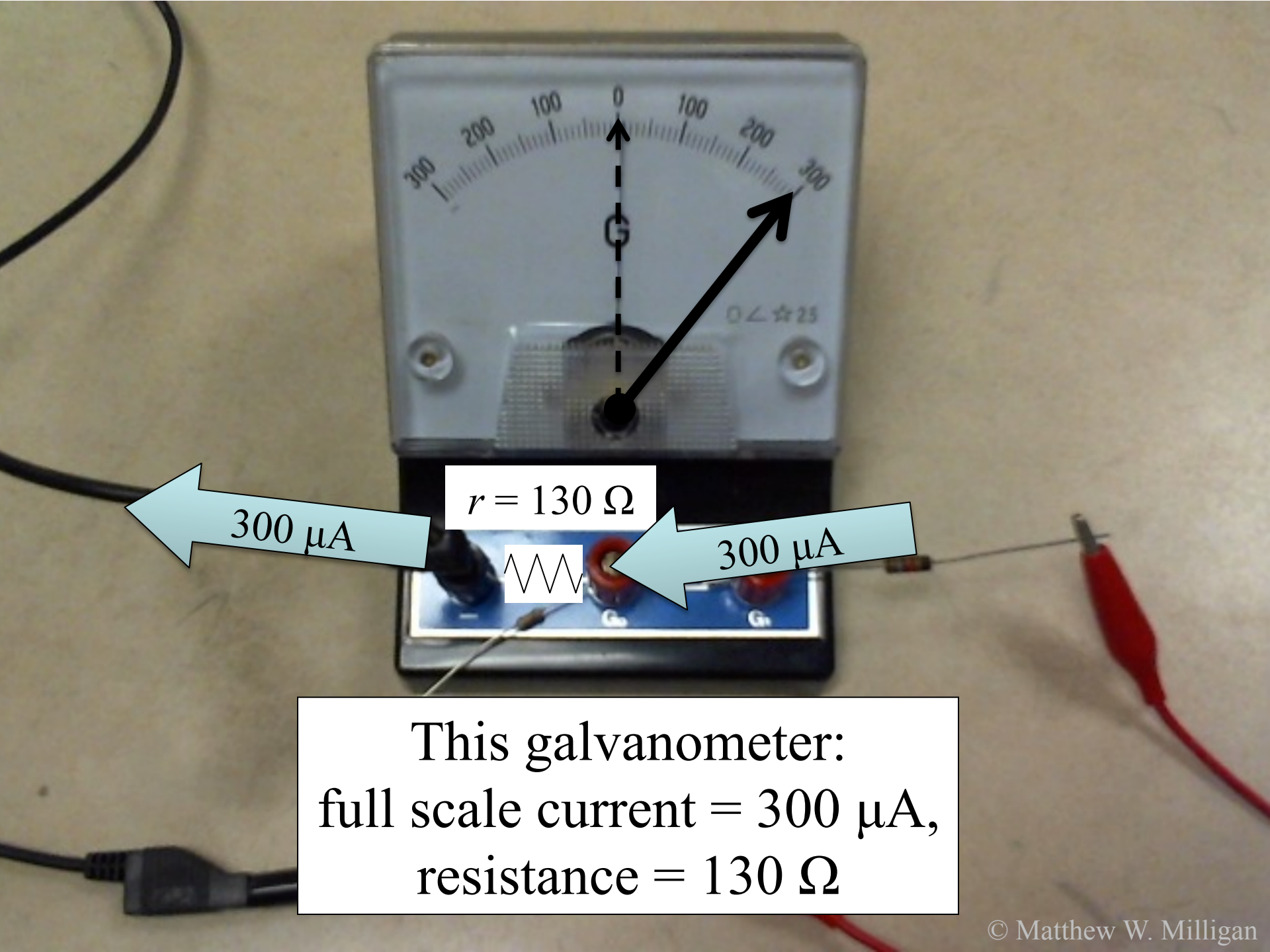

$r = 130 \Omega$



$300 \mu\text{A}$

$300 \mu\text{A}$

This galvanometer:
full scale current = $300 \mu\text{A}$,
resistance = 130Ω

What value resistors would turn the galvanometer into a voltmeter with two ranges:

full scale = $300 \mu\text{A}$
resistance = 130Ω

$R = 2.4 \text{ k}\Omega$

$R_1 = ?$

0 to 3 V

What value resistors would turn the galvanometer into a voltmeter with two ranges:

full scale = $300 \mu\text{A}$
resistance = 130Ω

$R = 2.4 \text{ k}\Omega$



$R_2 = ?$

0 to 6 V

What value resistors would turn the galvanometer into a voltmeter with two ranges:

full scale = $300 \mu\text{A}$
resistance = 130Ω

$R = 2.4 \text{ k}\Omega$

$R_2 = 18 \text{ k}\Omega$


$R_1 = 10 \text{ k}\Omega$

0 to 6 V

0 to 3 V



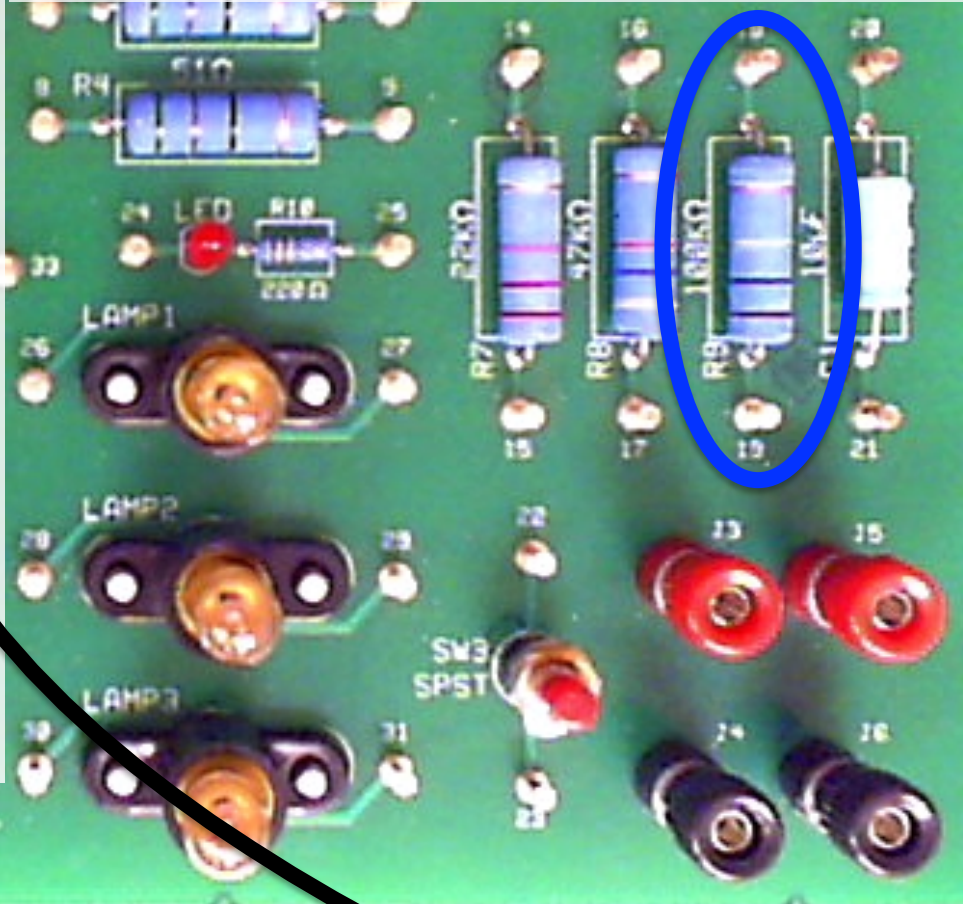If you use a 100 k Ω resistor instead of the 10 k Ω , what range of voltages can be measured? Try it...



Use your voltmeter to measure voltages of 1.5 V, 3.0 V or 6.0 V, being careful not to “peg the meter”.